

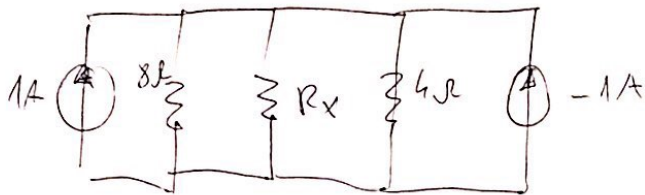
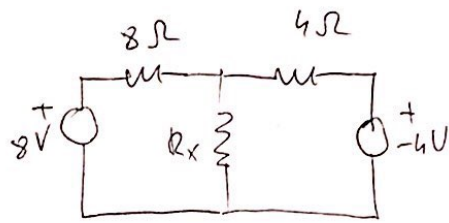


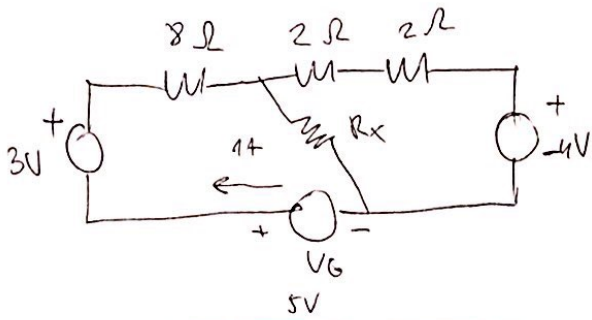① a)  $V_{AB} = 3V = U_T$       5)  $R_T = \frac{3 \cdot 6}{9} = 2 \Omega$       6)  $V_6 = 5V$   
 $R_T = 8 \Omega$        $U_T = -4V$



$U_{AD} = 0V$

$P_{R_p} = 0W$  zu blanko  $R_p$

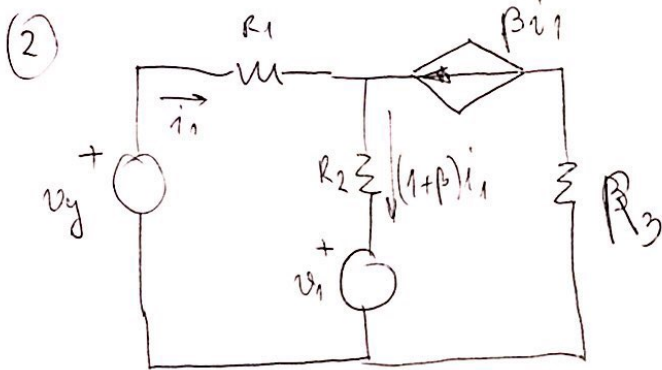


$$v_1 + (1+\beta) i_1 R_2 + i_1 R_1 = v_y$$

$$\frac{v_y - v_1}{R_1 + (1+\beta) R_2} = i_1$$

$$R_{EKV} = R_1 + (1+\beta) R_2$$
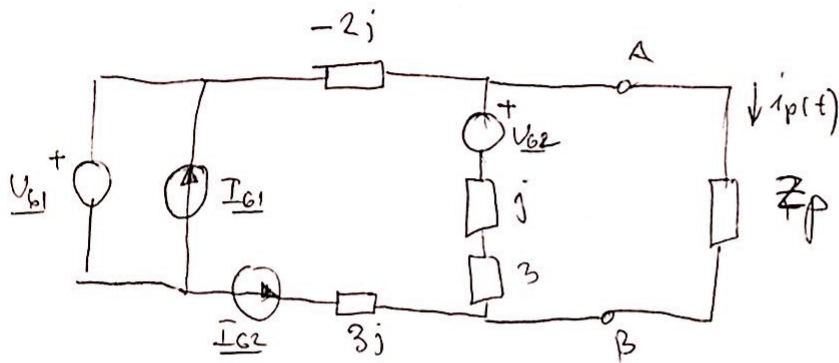
$$\underline{U}_{G1} = 1+j \quad \underline{U}_{G2} = 2j \quad \underline{I}_{G1} = 1-j \quad I_{G2} = j$$



$$U_{AB} = -I_{G2}(3+j) + U_{G2} = -3j + 1 + 2j = 1-j$$

$$R_{Th} \quad Z_T = 3+j$$

$$I_N = \frac{1-j}{3+j} \cdot \frac{3-j}{3-j} = \frac{3-3j-j-1}{10} = \frac{2-4j}{10} = \frac{1}{5} - \frac{2}{5}j$$

$$\underline{I}_N = \frac{1}{5} - \frac{2}{5}j \quad Z_N = 3+j$$

$$Z_P = 3-j \quad R_P = 3 \Omega \quad C_P = 31.8 \mu F$$

$$(3+j)(1-2j) = 3+j-6j+2 = 5-5j$$


$$I_P = \frac{Z_N}{Z_N + Z_P} \cdot I_N = \frac{3+j}{6} \cdot \frac{1}{5} (1-2j) = \frac{1-j}{6}$$

$$\underline{I}_P = \frac{1}{6} - \frac{1}{6}j \quad \frac{\sqrt{2}}{6} \left( \frac{\sqrt{2}}{2} - \frac{\sqrt{2}}{2}j \right) = \frac{\sqrt{2}}{6} e^{-45^\circ}$$

$$\frac{2}{36} = \frac{1}{18}$$

$$i_p(t) = \frac{1}{3} \cos(\omega t - 45^\circ)$$
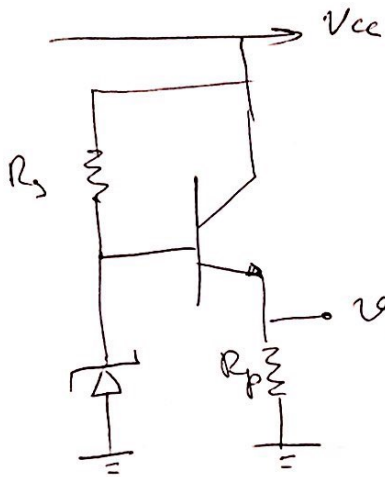
$$\underline{S} = \frac{3}{18} - \frac{j}{18} = \frac{1}{6} - \frac{j}{18} \quad P = \frac{1}{6} W \quad Q = -\frac{1}{18} VAR$$



3a  $V_{cc} \in (0, 0,6V)$  Q je završ, DZ: OFF

$V_{cc} > 0,2V$



$V_{CE} = V_{CES}$   
 $V_{BE} = V_{BES}$   
 $i_c < \beta i_b$

$V_i = 0V$

~~$V_{cc} - R_s i_b - V_{BE} - i_e R_p = 0$~~

~~$V_e = V_{cc} - V_{CES} = V_{cc} - V_{CES}$   
 $i_e = \frac{V_{cc} - V_{CES}}{R_p}$~~

~~$V_{cc} - R_s i_b - V_{BE} - V_{cc} + V_{CES} = 0$~~

$\frac{V_{cc} - V_B}{R_s} = i_b$   
 $V_B = V_{cc} - R_s i_b$

~~$i_b = \frac{V_{CES} - V_{BE}}{R_s}$~~

$V_{cc} - R_s i_b - V_{BE} - i_e R_p = 0$

$V_i = V_{cc} - V_{CES}$

$i_b = \frac{V_{cc} - V_{BE} - i_e R_p}{R_s} = \frac{V_{CES} - V_{BE}}{R_s} < 0$

$V_x - V_{cc} = i_b R_s$

$V_{cc} - R_s i_b - V_{BE} - (1 + \beta) i_b \cdot R_p$

$i_b = \frac{V_{cc} - V_{BE}}{R_s + (1 + \beta) R_p} < 0$

$V_i = \frac{V_{cc} - V_{BE}}{R_s + (1 + \beta) R_p} \cdot (1 + \beta) R_p$

3a  $V_{cc} > 0,6V$  Q → gap DZ: OFF

$V_i = \frac{V_{cc}}{2} - 0,3V$

$i_{CE} = V_{cc} - \frac{V_{cc}}{2} + 0,3V = \frac{V_{cc}}{2} + 0,3V$


~~$V_B = i_b R_s - V_{cc} = \frac{V_{cc} - V_{BE}}{R_s + (1 + \beta) R_p} \cdot R_s - V_{cc} = \frac{1}{2} V_{cc} - \frac{1}{2} V_{BE} + V_{cc} = \frac{1}{2} V_{cc} - \frac{1}{2} V_{BE}$~~

3a  $V_B = \frac{1}{2} V_{cc} - 0,3$   $V_B = \frac{1}{2} V_{cc} + 0,3V$


3a  $V_{cc} = 9,4V$  DZ → upredoi  $V_i = 4,4V$

5

DC :

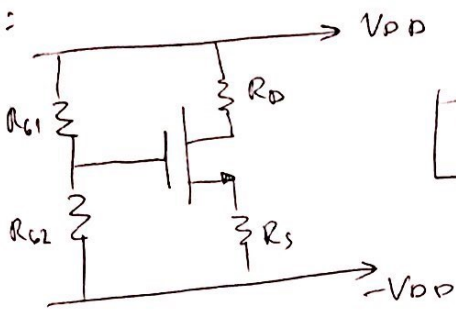

$V_G = 0V$

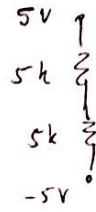

$5V - 5k \cdot 1\mu A = 0$

$V_{GS} = 1 = \frac{10V}{10k\Omega} = 1\mu A$

~~$I_{D1} = \frac{\beta}{2} (V_{GS})^2$     $I_D = \frac{\beta}{2} (-V_S - V_t)^2$~~

~~$\frac{V_S - V_{DD}}{R_S} = I_D$     $V_S = R_S I_D + V_- = R_S I_D - 5V$~~

~~$I_D = \frac{\beta}{2} (-R_S I_D + 5V - 3V)^2$~~

~~$1000 I_D = (2 - 2000 I_D)^2$~~

~~$2000^2 I_D^2 - 9000 I_D + 4 = 0$~~

~~$I_{D1/2} = \frac{9000 \pm 8062,25}{2 \cdot 2000^2}$~~

~~$I_{D1} = 2,13mA$     $I_{D2} =$~~

~~$-5 + R_S I_D = V_S$~~

$I_D = \frac{\beta}{2} (-V_S - V_t)^2$

$I_D = \frac{\beta}{2} (5 - R_S I_D - V_t)^2$

$2000^2 I_D^2 - 8000 I_D + 4 = 1000 I_D$

$1000 I_D = (2 - 2000 I_D)^2$

$2000^2 I_D^2 - 9000 I_D + 4 = 0$     $I_{D1/2} = \frac{9000 \pm 4123}{2 \cdot 2000^2}$

$I_{D1} = 1,64mA$

$I_{D2} = 0,61mA$


$V_{S1} = -1,72V$

$V_{S2} = -3,78V \Rightarrow V_{GS} > V_T$

$V_D = 1,95V \Rightarrow V_{GD} < V_T$

$g_m = 1,562mS$

$$g_m = 1,562 \text{ mS}$$

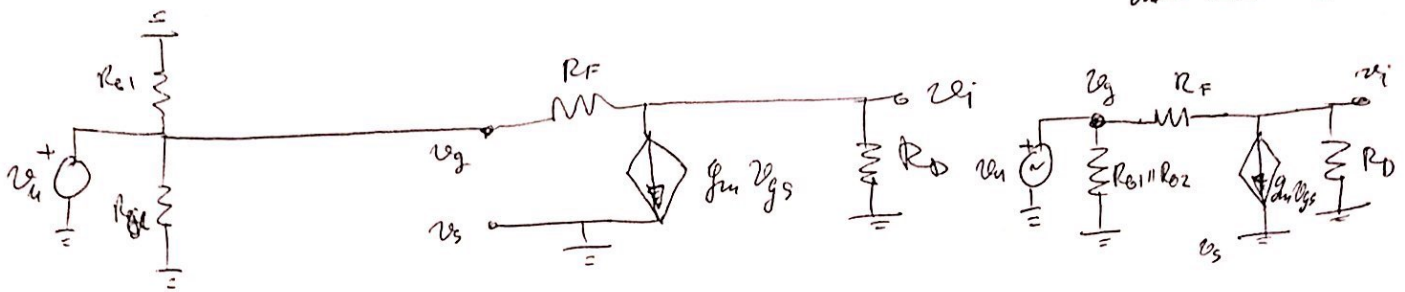

$$v_{gs} = v_u$$

$$\frac{v_g - v_i}{R_F} + \frac{0 - v_i}{R_D} = g_m v_g / -R_D R_F$$

$$v_g \cdot R_D - v_i \cdot R_D - v_i \cdot R_F = g_m R_D R_F \cdot v_g$$

$$v_g \cdot R_D (1 - g_m R_F) = v_i (R_D + R_F)$$

$$v_i = \frac{R_D (1 - g_m R_F)}{R_D + R_F} v_g \quad a$$

$$v_g - v_i = v_g \left( 1 - \frac{R_D (1 - g_m R_F)}{R_D + R_F} \right) = v_g (1 - a_v)$$

$$= v_g \left( \frac{R_D + R_F - R_D (1 - g_m R_F)}{R_D + R_F} \right) = v_g$$

$$i_1 = \frac{v_g (1 - a_v)}{R_F} \quad i_2 = \frac{v_g}{R_{g1} || R_{g2}}$$

$$i_u = v_g \left( \frac{1 - a_v}{R_F} + \frac{1}{R_{g1} || R_{g2}} \right)$$

$$R_{UL} = \frac{R_F}{1 - a_v} || R_{g1} || R_{g2} = \frac{R_F}{1 - a_v} || 2,5 \text{ k}\Omega =$$


$$\frac{R_D (1 - g_m R_F)}{R_D + R_F} = -4$$

$$R_D - 6,24 R_F = -4 R_D - 4 R_F$$

$$5 R_D = 2,24 R_F$$

$$R_F = 8,928 \text{ k}\Omega$$

$$R_{UL} = 1042 \Omega$$

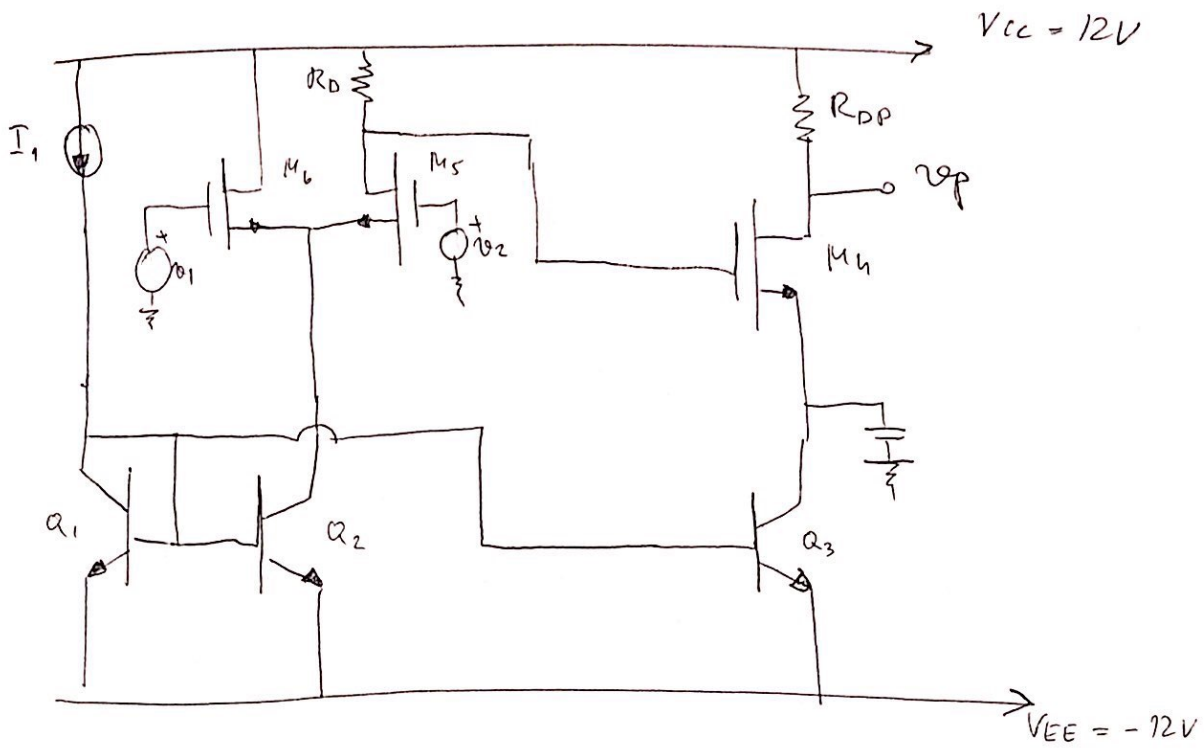

$$3I_B + I_C = I_1$$

$$(\beta + 3)I_B = I_1$$

$$I_1 = \frac{\beta + 3}{\beta} \cdot 1\text{mA} = 1,03\text{mA}$$

$$I_6 = I_5 = \frac{I_C}{2} = 0,505\text{mA} \Rightarrow g_{m5} = g_{m6} = \sqrt{2I_D \cdot \beta} = 3,2\text{mA/V} \approx 1\text{mS}$$

$$I_4 = I_C \Rightarrow g_{m4} = \sqrt{2I_C \cdot \beta} = 1,41\text{mS}$$

$$I_4 = 1\text{mA} \quad V_{GS4} = \sqrt{\frac{2I_4}{\beta}} + V_t \quad V_{G4} = \sqrt{\frac{2I_4}{\beta}} + V_t + V_s = -1,59\text{V}$$



$$R_{DP} = 12\text{k}\Omega, \quad \frac{V_{CC} - V_{G4}}{\frac{I_C}{2}} = R_D = 27,18\text{k}\Omega$$

$$v_{g1} = 0,1\text{mV} \cos \omega t \quad v_{g2} = -0,12\text{mV} \cos(\omega t + \frac{\pi}{4})$$

$$\underline{V_{G1}} = \frac{0,1}{\sqrt{2}} \quad \underline{V_{G2}} = -\frac{0,12}{\sqrt{2}} \cdot \left(\frac{\sqrt{3}}{2} + \frac{1}{2}j\right)$$

$$\frac{0,1}{\sqrt{2}} + \frac{0,12}{\sqrt{2}} \left(\frac{\sqrt{3}}{2} + \frac{1}{2}j\right) = \frac{0,1}{\sqrt{2}} (1 + \sqrt{3} + j)$$
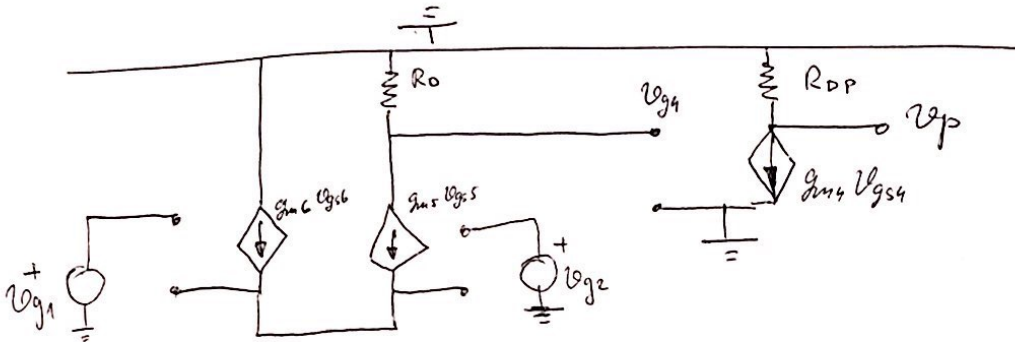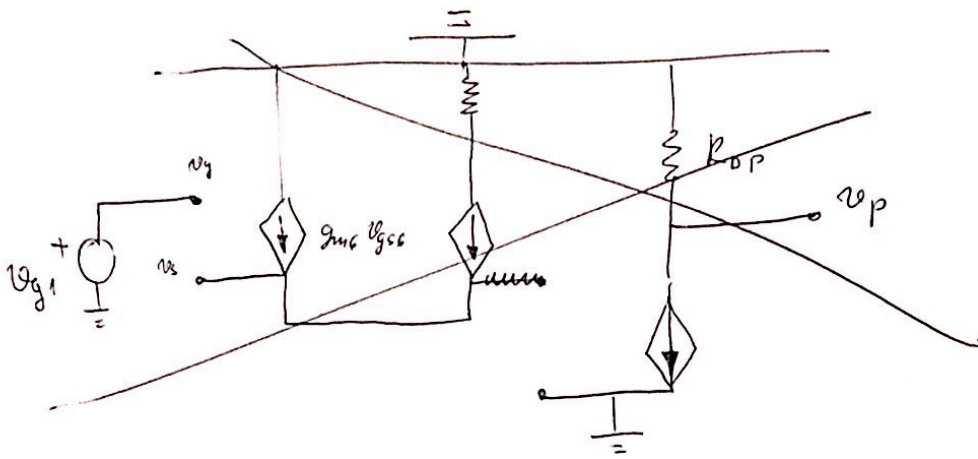
$$\underline{V_{G1}} - \underline{V_{G2}} = \frac{0,1}{\sqrt{2}} (1 + \sqrt{3} + j) \quad V_{\text{diff}} = 0,1$$



$$v_{gs5} = v_{gs6}$$

$$g_m v_{g1} - g_m v_{s1} + g_m v_{g2} - g_m v_{s2} = 0$$

$$g_m v_{gs6} = -g_m v_{gs5}$$

$$v_{s1} = \frac{v_{g2} + v_{g1}}{2}$$

$$v_{G6} = -v_{G5}$$

$$v_{g1} = -v_{g2}$$

$$v_{g4} = -g_m \left( v_{G2} - \frac{v_{g2} + v_{g1}}{2} \right) R_D$$

$$v_{g4} = -g_m \cdot \frac{v_{g2} - v_{g1}}{2} R_D$$



$$v_p = \frac{+g_{m4} \cdot g_m \cdot R_D \cdot R_p}{2} \cdot (v_{g2} - v_{g1})$$

$$v_f = - \frac{g_m g_{m4} R_D R_p}{2} (v_{g1} - v_{g2})$$

$$a \approx -230$$

ped '19

7

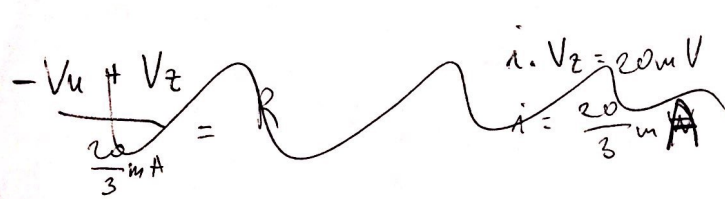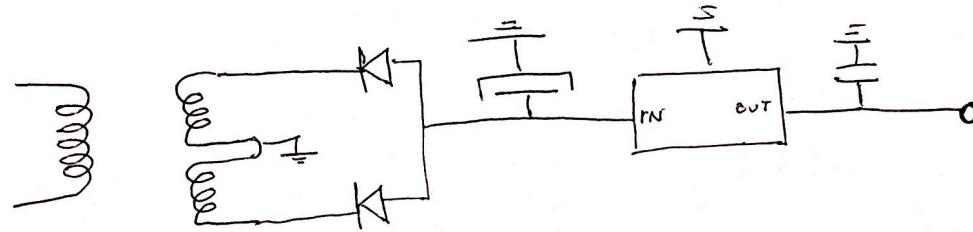

$$i = \frac{20}{3} \text{ mA}$$

$$\frac{V_z - V_u}{\frac{20}{3} \text{ mA}} = 1050 \Omega$$

$$R_2 = 2 \text{ k}\Omega \quad 1 \text{ mA}$$

$$i_{\text{max}} = 10 \text{ mA}$$

$$\frac{-3 - V_{u\text{max}}}{1050} = 10 \text{ mA}$$

$$V_{u\text{min}} = -13.5 \text{ V}$$

$$V_i - V_u < 0.2$$

$$V_{u\text{max}} = -5.2 \text{ V}$$