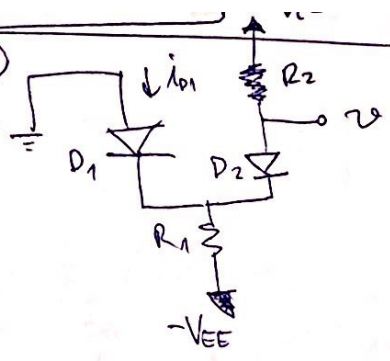



$$i_D = I_S \left( e^{\frac{V_D}{V_T}} - 1 \right)$$

(51) a)



$$V_{CC} = V_{EE} = 10V$$

$$R_2 = 2R_1 = 10k\Omega$$

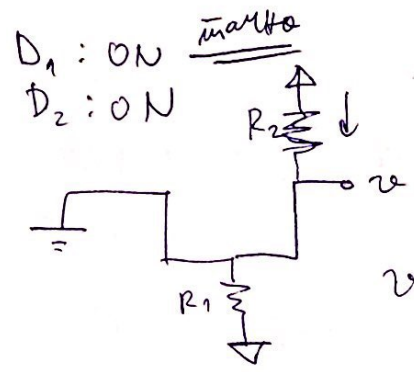

$$v = 0V \quad i_{D2} = i_{R2} = \frac{V_{CC}}{R_2} > 0$$

$$i_{R1} = \frac{v - (-V_{EE})}{R_1} > 0$$


$$i_{D2} = 1mA$$

$$i_{R1} = \frac{10}{5k\Omega} = 2mA$$

$$i_{D1} = i_{R1} - i_{D2} \Rightarrow 0$$

$$i_{D1} = i_{D2} = 1mA$$

a)  $R_1 = 2R_2 = 10k\Omega$

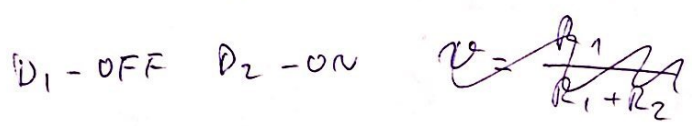

$$v = \frac{R_1}{R_1 + R_2} \frac{V_{CC} - V_{EE}}{R_2} = \frac{V_{CC} - V_{EE}}{R_2}$$

$$R_1 v - R_2 v = R_2 v + R_2 v \quad v(R_1 - R_2) = 2v(R_1 + R_2)$$


$$v = \frac{R_1 - R_2}{R_1 + R_2} V = \frac{1}{3} V = 3.33V$$

$$V_{D1} = -3.33V < 0$$


$$i_{D2} = \frac{V_{CC} - v}{R_2} = 1.33mA$$

$$i_{D1} = 0$$


52

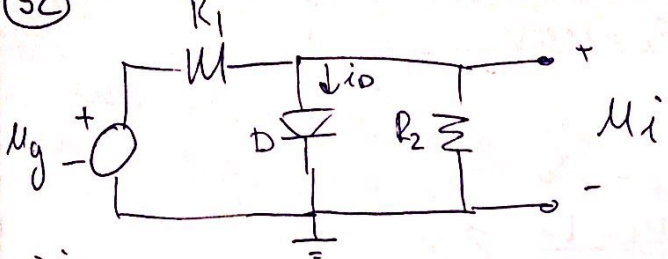


$0 \leq U_g \leq 5V$

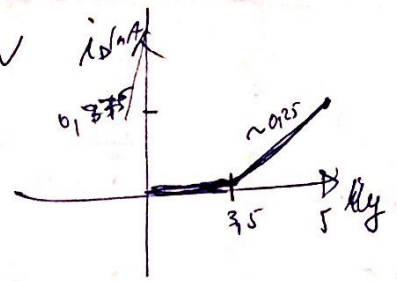


2. case:  
 $U_g = 0$  D = OFF

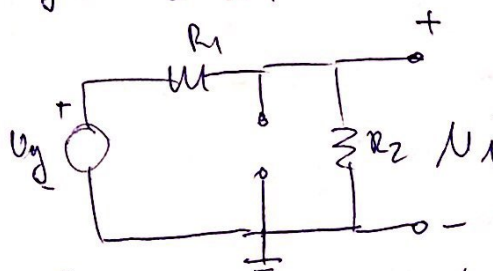

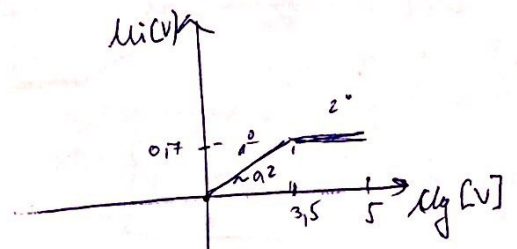$i_{i0} = i_i = \frac{R_2}{R_1 + R_2} U_g$   
 $U_D < V_D$



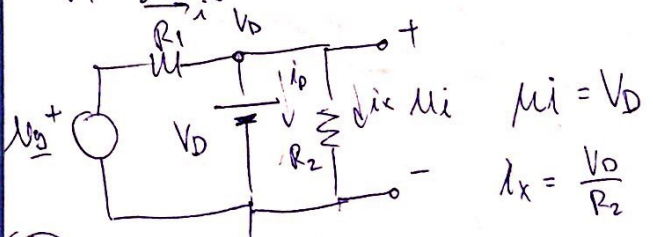
$\frac{R_2}{R_1 + R_2} = \frac{1}{5}$   $0.17 = \frac{1}{5} U_g$   $U_D = \frac{R_2}{R_1 + R_2} U_g$   $U_D < V_D$   $U_g = 5V$




$i_i = V_D$   
 $i_x = \frac{V_D}{R_2}$

$i_{R1} = i_D + i_x$   
 $i_{R1} = \frac{U_g - V_D}{R_1}$   $i_D = \frac{U_g - V_D}{R_1} - \frac{V_D}{R_2} = \frac{1}{4} kU_g - 0.875$


53

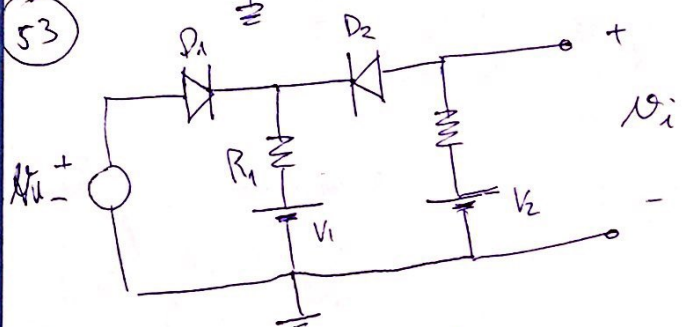

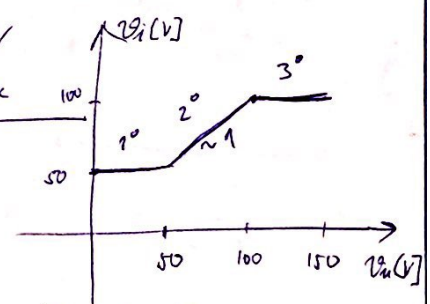$0 \leq U_u \leq 150V$   
 $V_1 = 25V$   $V_2 = 100V$   
 $R_1 = 100k$   $R_2 = 200k$



$U_u = 0$   $D_1$ : OFF  $D_2$ : ON

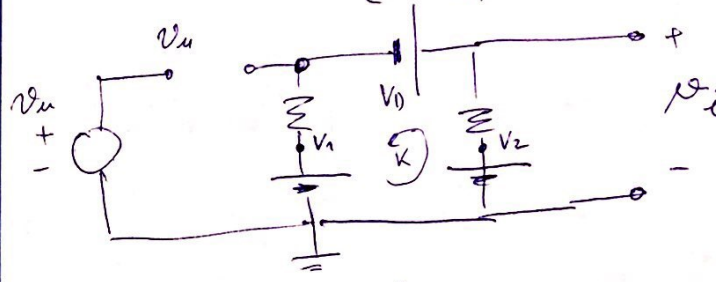


$+V_2 - i_D(R_2 + R_1) + V_D - V_1 = 0$   
 $i_D = \frac{V_2 - V_1}{R_2 + R_1} > 0$

$i_D \cdot R_1 = V_k - V_1$   
 $V_k = i_D R_1 + V_1 = \frac{V_2 - V_1}{R_2 + R_1} R_1 + V_1 = \frac{75}{300k} \cdot 100k + 25 = 50V$

$U_{D1} = U_u - 50V$


2. case:

$D_1$ : ON,  $D_2$ : ON

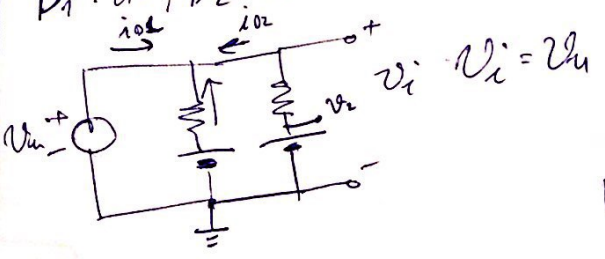

$i_{D2} = \frac{U_u - U_u}{R_2}$   
 $i_{D1} = - \left( \frac{U_u - U_u}{R_1} + \frac{U_u - U_u}{R_2} \right) = \frac{U_u - U_u}{R_1} + \frac{U_u - U_u}{R_2}$

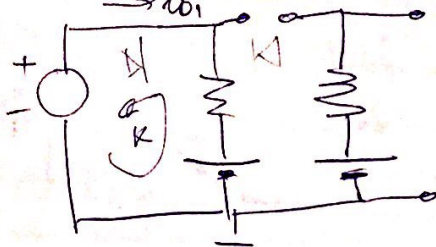$D_2$  te invarian OFF za  $U_u = U_u = 100V$



$$v_i = v_2 = 100V$$


$$V_1 + i_{o1} \cdot R_1 - v_o = 0$$

$$i_{o1} = \frac{v_o - V_1}{R_1} \rightarrow$$

$$v_{D2} = v_2 - v_o < V_D$$

D<sub>1</sub> state ON  
D<sub>2</sub> state OFF


54

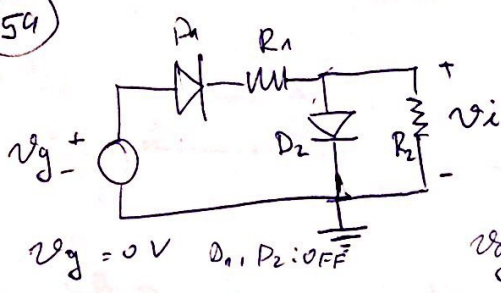


$$0 \leq v_g \leq 5V$$

$$V_D = 0.6V$$

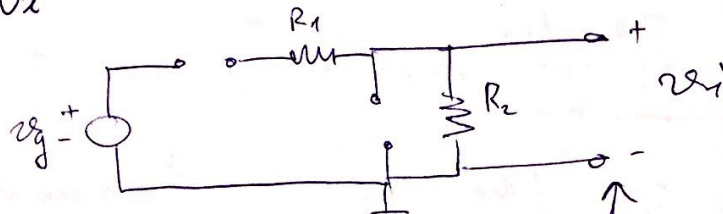$v_g = 0V$  D<sub>1</sub>, D<sub>2</sub>: OFF



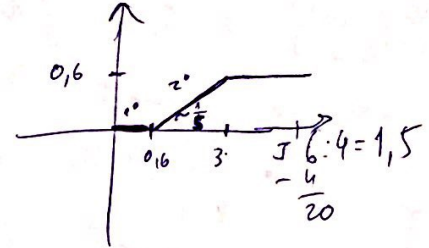
$$v_i = v_o \cdot \frac{R_2}{R_1 + R_2} = \frac{1}{4} v_o \Rightarrow 0V = v_i$$



$$v_{D1} = v_g \quad v_{D2} = 0V$$

D<sub>1</sub> state ON za  $v_g = 0.6V$

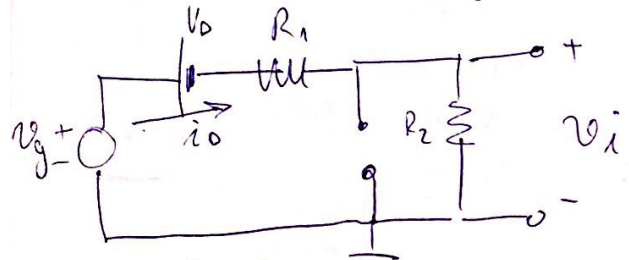


$$v_i = (v_g - V_D) \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1}{4}$$

$$v_{D2} = v_i \rightarrow$$

D<sub>2</sub> state OFF za  $v_i = V_D \Rightarrow (v_g - V_D) \frac{R_2}{R_1 + R_2} = V_D$

$$i_o = \frac{v_g - V_D}{R_1 + R_2} \rightarrow D_1 \text{ state ON}$$
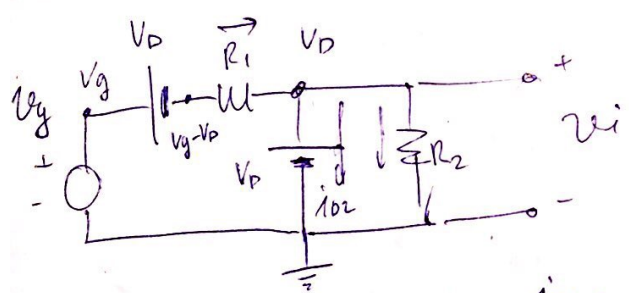
$$v_g = V_D \left( 1 + \frac{R_1}{R_2} \right) = 0.6 \cdot \frac{5}{4} = 0.75 \cdot 5 = 3.75V$$



$$i_{R2} = \frac{V_D}{R_2} \quad i_{o2} =$$



$$i_{o1} = \frac{v_g - 2V_D}{R_1} \rightarrow$$

$$i_{o2} + i_{R2} = i_{o1}$$


$$i_{o2} = i_{o1} - i_{R2}$$

$$i_{o2} = \frac{v_g - 2V_D}{R_1} - \frac{V_D}{R_2} \rightarrow$$


state ON

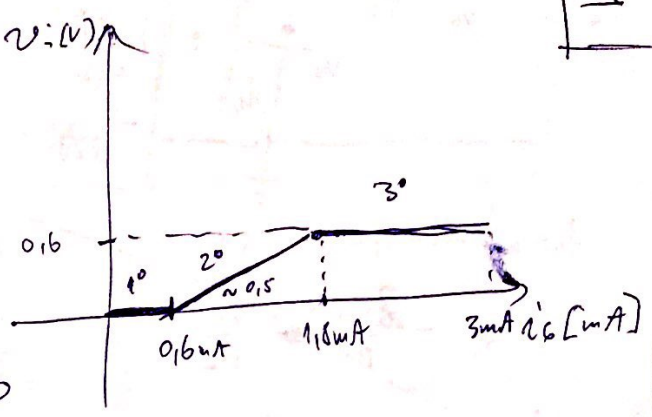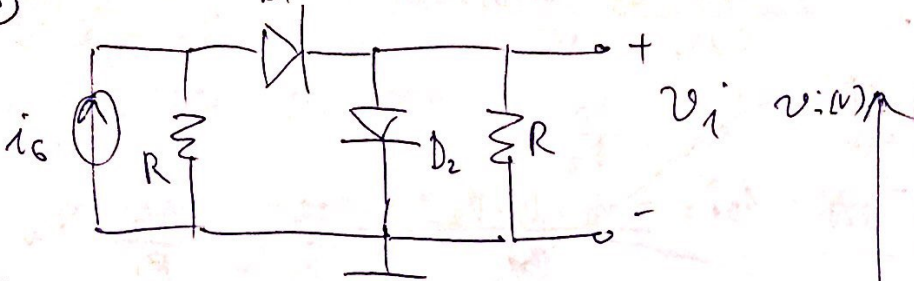

$i_G = 0$   $D_1: OFF, D_2: OFF$

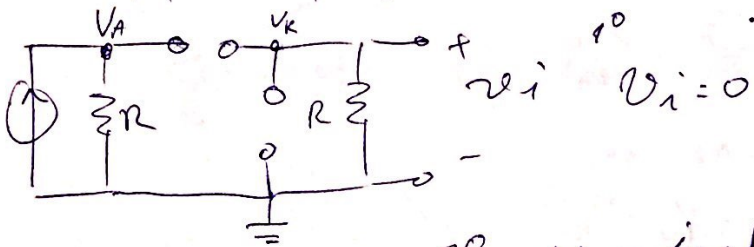

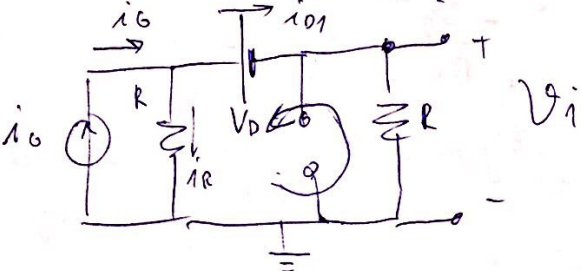$V_{D2} = 0, V_{D1} = V_A - V_K \rightarrow 0$   $V_A = i_g \cdot R \rightarrow$   $\text{zau } i_g = 0,1 \text{ mA}$   $D1 \text{ e}$   
 $\text{izostajiva}$




$i_{D1} \cdot R + V_D - i_g \cdot R = 0$   $i_{D1} + i_R = i_g$   
 $i_{D1} R + V_D + i_{D1} R - i_g R = 0$   $i_R = i_g - i_{D1}$   
 $i_{D1} = i_g - \frac{V_D}{R}$


$i_{D1} \cdot R + V_D - i_g R + i_{D1} R = 0$   $v_i = v_{D1} = i_{D1} R = i_g R - V_D$

$i_{D1} = \frac{i_g}{2} = \frac{1}{2} \frac{V_D}{R} = \frac{1}{2} i_g + 0,13 \text{ mA}$

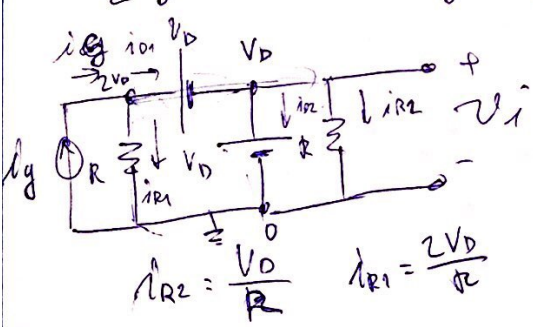$v_i = \frac{1}{2} i_g R = 0,13 \text{ V}$   $V_D = \frac{1}{2} i_g R = 0,13 \text{ V}$   $i_g R = 0,13 \text{ V}$   
 $i_g = 1,8 \text{ mA}$



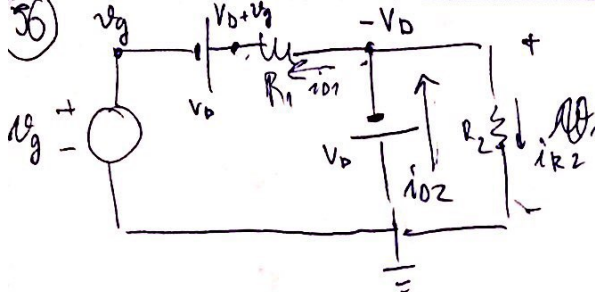$v_i = \frac{V_D}{R}$   
 $i_{D1} = i_g - i_{R1} = i_g - \frac{2V_D}{R}$   $D_1, D_2 \text{ - vanaju 0V}$   
 $i_{D2} = i_{D1} - i_{R2} = i_g - \frac{3V_D}{R}$



$v_g = -5V$      $D_1, D_2 : ON$   
 $i_{D1} = -V_D$   
 $i_{D2} = -\frac{V_D}{R_2}$   
 $i_{D1} = \frac{-V_D - V_D - v_g}{R_1} = -\frac{v_g}{R_1} - \frac{2V_D}{R_1}$


$i_{D2} = i_{D1} + i_{D2}$   
 $= -\frac{v_g}{R_1} - \frac{2V_D}{R_1} - \frac{V_D}{R_2}$

$i_{D1}' = \frac{5}{3} - \frac{1,2}{3} = \frac{3,8}{3} mA > 0$   
 $-\frac{v_g}{R_1} = \frac{2V_D}{R_1}$      $v_g = -2V_D = -1,2V$

$v_g = -2V_D - \frac{V_D}{R_2} \cdot R_1 = -1,2 - 0,2 = -1,4V$


$i_{R2} = -\frac{V_D}{R_2}$      $i_{D1} = \frac{-V_D - V_D - v_g}{R_1}$

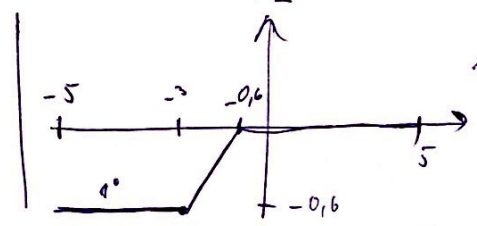$i_{D2} = i_{D1} + i_{R2} =$   
 $= -\frac{v_g}{R_1} - \frac{2V_D}{R_1} - \frac{V_D}{R_2}$



$v_g = -2V_D = -1,2V$

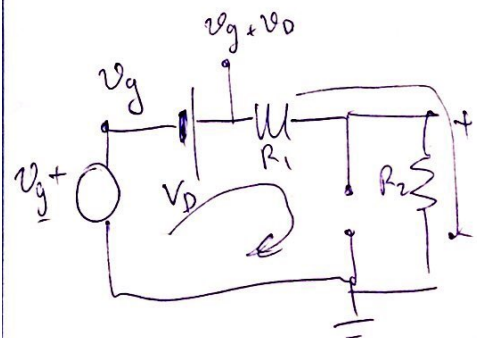$v_g = -2V_D - \frac{R_1}{R_2} V_D = -1,2 - 1,8V = -3V$




$v_i = (v_g + v_D) \frac{R_2}{R_1 + R_2}$

$i_{D1} = \frac{v_g + v_D}{R_1 + R_2}$      $\Rightarrow v_g = -V_D$   
 $D_1 \rightarrow OFF$

$v_{D1} = \frac{v_g + v_D}{R_1 + R_2} \cdot R_2 = \frac{1}{4} v_g + \frac{1}{4} v_D =$

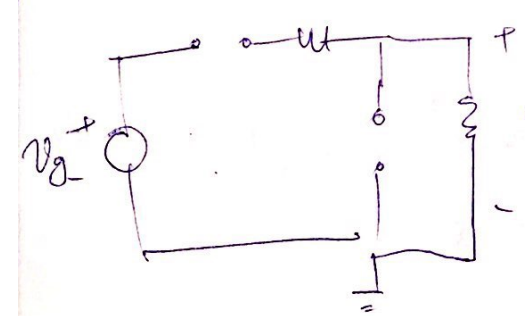$v_D = -\frac{1}{4} v_g - \frac{1}{4} v_D$



$v_{D2} = 0$   
 $v_i = 0$   
 $v_{D1} = -v_g$   
 $v_i = 0$


57

B4

$i_g = -2 \mu A$

$D_1 : ON, D_2 : OFF$



$V_i = -\frac{V_D}{R_2}$

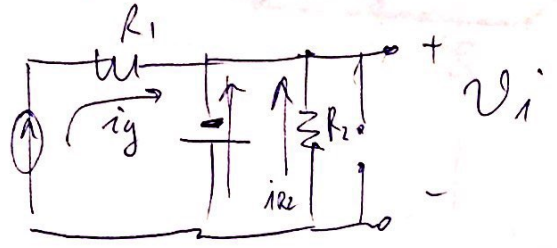


$V_{D2} = -V_D < V_D$

$i_{R2} = \frac{V_D}{R_2}$      $i_{D1} = -i_g - i_{R2} = -i_g - \frac{V_D}{R_2} = 2 - 0.6 \mu A > 0$

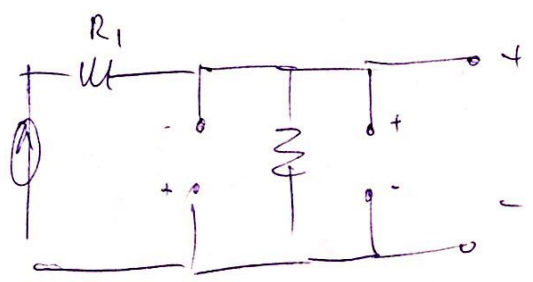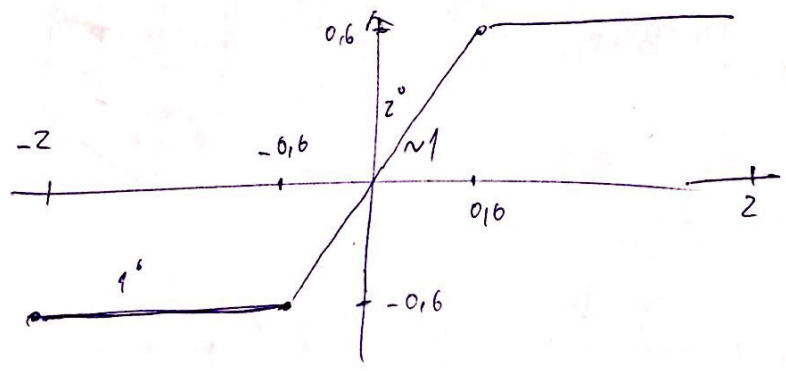$i_{D1} = -i_g - \frac{V_D}{R_2} \rightarrow D_1 \rightarrow OFF$      $i_g = -\frac{V_D}{R_2} = 2$




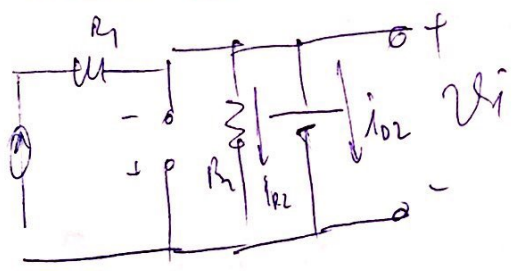
$V_i = i_g R_2$   
 3a  $V_{D2} = V_D$      $D_2 \rightarrow ON$      $i_g = 0.6 \mu A$



$i_{R2} = \frac{V_D}{R_2}$      $i_{D2} = i_g = i_{R2}$   
 $D_2$  on,  $D_1$  off


19

50

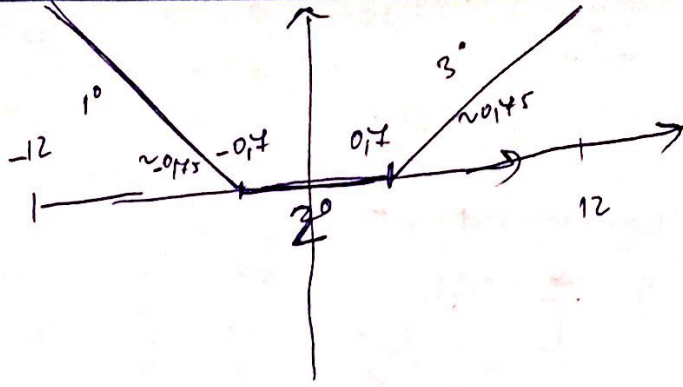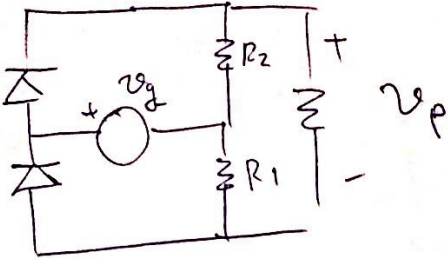

$v_g = -12V$

$D_1 : ON \quad D_2 : OFF$

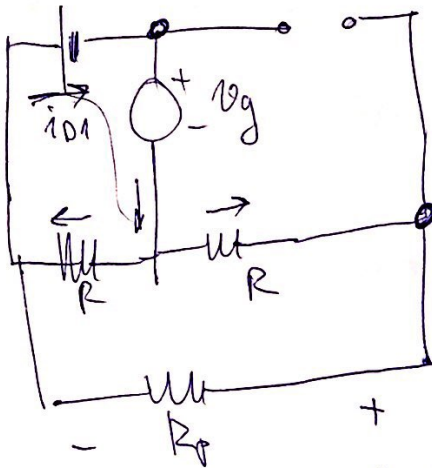


$v_g = -V_p$

$i_{D1} = - \frac{v_g + V_D}{R + (R + R_p)}$

$R || (R + R_p) = 1 || 4 = \frac{4}{5} k\Omega$

$i_x = i_D +$

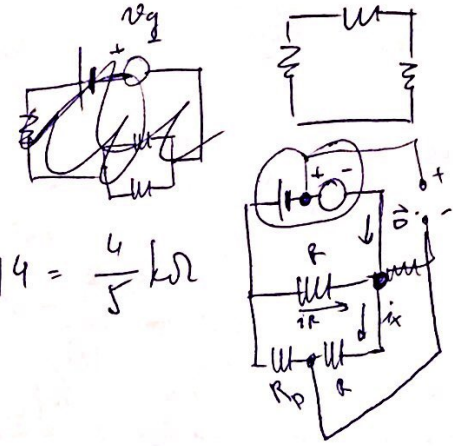

$1 || 4 = \frac{1 \cdot 4}{1+4} = \frac{4}{5}$


$\frac{v_g + V_D}{R} + \frac{v_g + V_D}{R + R_p} = (v_g + V_D) \left( \frac{1}{1} + \frac{1}{4} \right)$

$i_D = - \frac{5}{4} \cdot v_g - \frac{5}{4} \cdot V_D$

$i_x = - \frac{v_g + V_D}{R + R_p} \Rightarrow \boxed{v_p = - \frac{3}{4} (v_g + V_D)}$

$3v_g = V_D$   
 $v_g = \frac{V_D}{3}$

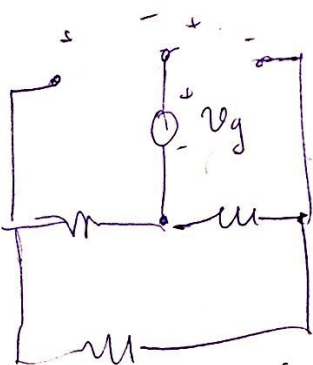$-\frac{1}{4} (v_g + V_D) + v_g = \frac{V_D}{3} \Rightarrow v_{D2} = \frac{3}{4} v_g - \frac{1}{4} V_D$




$v_p = 0$

3a  $v_g = 0.7V \quad D_2 \rightarrow ON$

$v_p = \frac{v_g - V_D}{R + R_p} \cdot R_p$

$i_{D2} = \frac{v_g - V_D}{R + (R + R_p)} = \frac{v_g - V_D}{4}$

$v_{D2} < V_D$

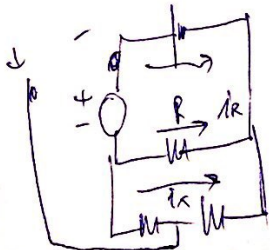

$i_x = - (i_{D2} + i_R)$

$i_x = - \frac{(v_g - V_D)}{R + R_p}$



$v_{D2} = -v_g + \left( \frac{v_g - V_D}{R + R_p} \right) R = -v_g + \frac{1}{4} v_g - \frac{1}{4} V_D$

59)  $v_g = -10V$

DZ, D: ON

1°


$v_p = -V_D$

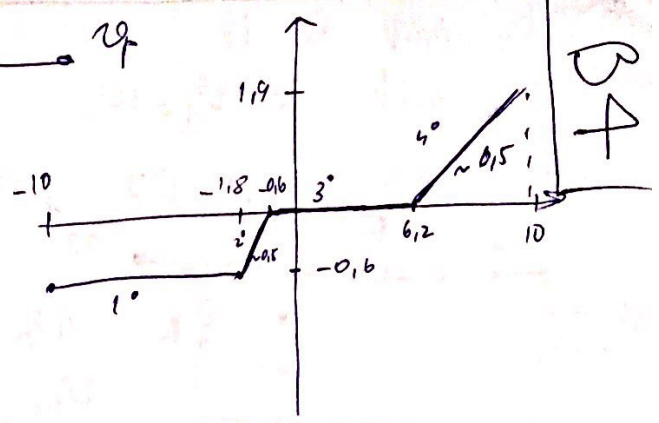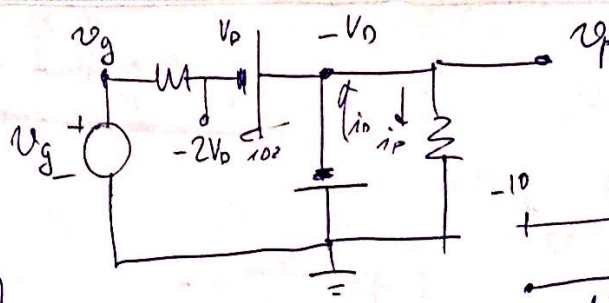

$i_{DZ} = \frac{-2V_D - v_g}{R} \rightarrow v_g = -2V_D = -1,2V$

$i_D = i_{DZ} + i_p = \frac{-2v_p - v_g}{R} - \frac{v_p}{R} = -\frac{v_g}{R} - \frac{3v_p}{R} \rightarrow v_g = -3v_p = -1,8V$

D → OFF

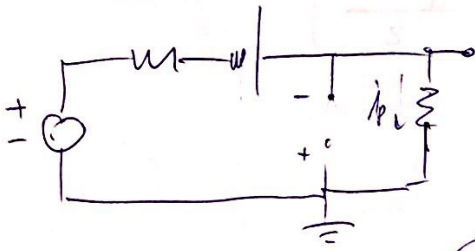


$i_p = \frac{v_g + v_p}{2R}$

$i_{DZ} = -\frac{v_g + v_D}{2R}$

$v_p = -i_p R = -\frac{v_g + v_p}{2}$

3a  $v_g = -v_p$   
DZ → OFF

$v_p = \frac{v_g - v_D}{2}$

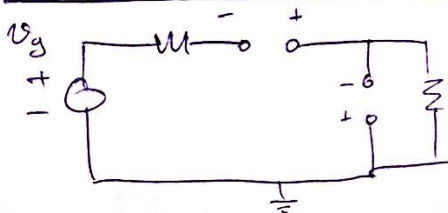


$v_D = 0$

$v_p = 0$

$v_{DZ} = -v_g$

3a  $v_g = -v_z$  DZ → OFF

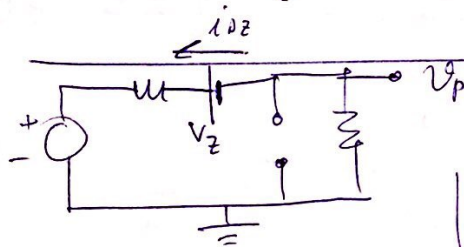


$i_{DZ} = \frac{v_z - v_g}{2R}$

$v_p = \frac{v_g - v_z}{2}$


$\frac{10 - 6,2}{2} = 5 - 3,1 = 1,9$



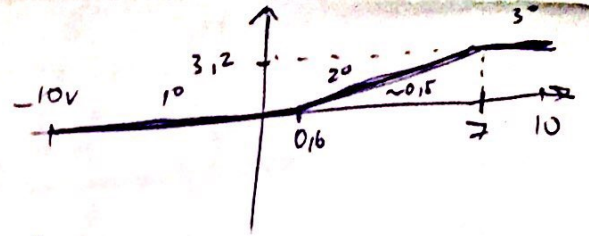
60)  $V_D = 0.6V$   $R = 1k$   
 $V_Z = 3.2V$   $-10 \leq V_g \leq 10$



$V_g = -10V \rightarrow D, DZ : OFF$

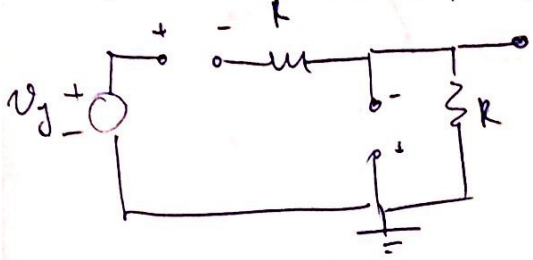

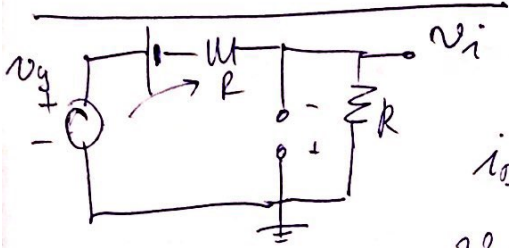
$V_D = V_g$   $V_{DZ} = 0V$   
 $V_i = 0V$   
 3a  $V_g = V_D \rightarrow ON$



$V_{DZ} = -V_i$   
 $i_D = \frac{V_g - V_D}{2R}$   $V_i = \frac{V_g - V_D}{2}$   
 $V_{DZ} = \frac{V_D - V_g}{2}$

3a  $\frac{V_D - V_g}{2} = -V_Z$   $DZ \rightarrow \text{on}$

$V_g = \frac{V_D}{2} + 2V_Z = 7V$

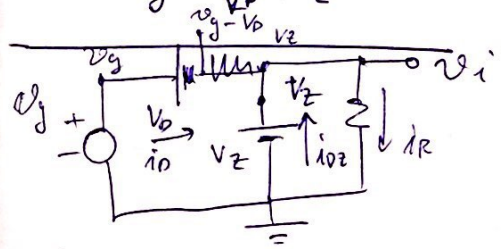

$V_i = \frac{V_Z}{2}$

$i_R = \frac{V_g}{R}$   $i_{DZ} = i_R - i_D = \frac{V_Z}{R} - \frac{V_g - V_D - V_Z}{R} < 0$   
 $\frac{V_g - V_D - V_Z}{R} = i_D$   $i_{DZ} \rightarrow$