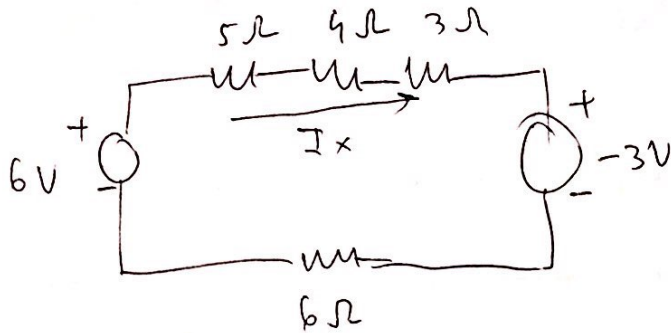


① a)

$$U_{AB} = 4 - 16 + 18 = 6V$$

$$R_{AB} = 5\Omega$$



d) $U_{CD} = 6V - 9V = -3V$


$$R_{CD} = 3\Omega$$

$$-3V + I_x(5+3+4+6) + 6 = 0$$

$$I_x = \frac{3}{18} = \frac{1}{6}A$$

$$P_{4\Omega} = 1W$$

②

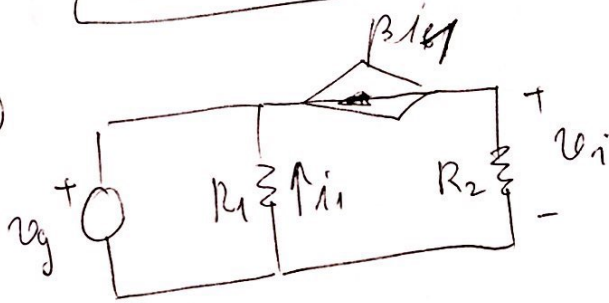


$$v_i = -\beta i_1 \cdot R_2$$

$$v_i = \beta \cdot \frac{R_2}{R_1} v_g$$

$$i_g = i_1(1+\beta)$$

$$i_1 = -\frac{v_g}{R_1}$$
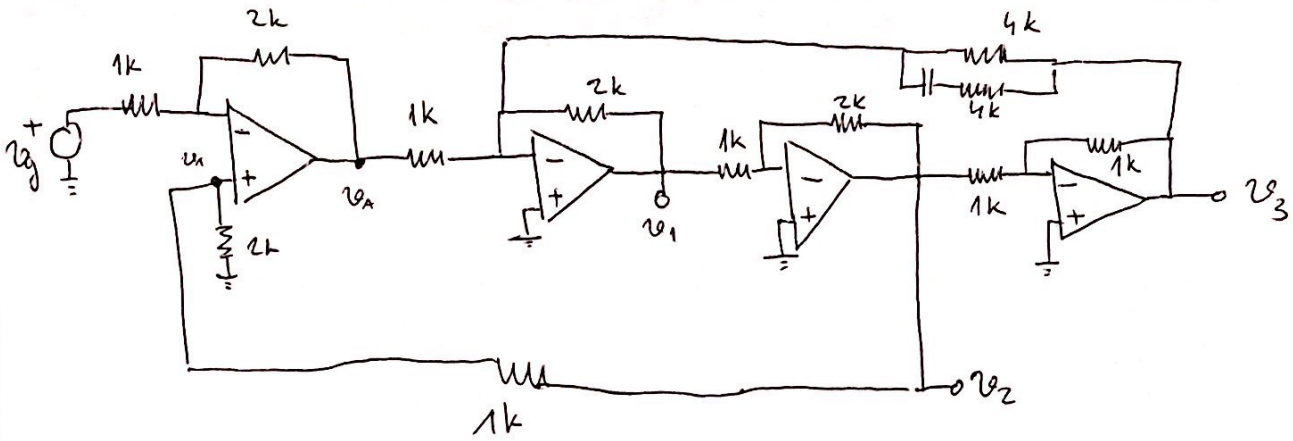
$$\frac{v_i}{v_g} = \beta \cdot \frac{R_2}{R_1}$$




AC: $v_x = \frac{2}{3} v_2$

$\frac{v_1}{1} = \frac{v_A - v_2}{2}$

$v_2 = -2v_1$

~~$v_2 = -2v_1$~~

$v_3 = -v_2 = 2v_1$

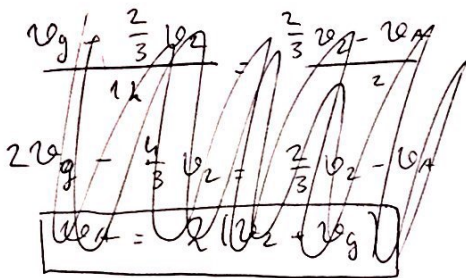

* $\frac{v_A}{1} = -\frac{v_1}{2} - \frac{v_3}{2}$

~~$v_1 + v_3 = -2v_A$~~

~~$3v_1 = -4v_2 = 4v_g$~~

~~$11v_1 = 4v_g$
 $v_1 = \frac{4}{11}v_g$~~

~~$-5v_1 = -4v_g$
 $v_1 = \frac{4}{5}v_g$~~

$v_1 + v_3 = -2v_A$
 $3v_1 = -4v_2 + 4v_g$
 $-5v_1 = 4v_g$

$v_1 = -\frac{4}{5}v_g$

$v_1 = -0,8 \sin \omega t$
 $v_2 = 1,6 \sin \omega t$
 $v_3 = -1,6 \sin \omega t$

$v_x = \frac{2}{3} v_2$

$\frac{v_g - \frac{2}{3}v_2}{1} = \frac{\frac{2}{3}v_2 - v_A}{2}$

$\frac{v_A}{1} = -\frac{v_1}{2} - \frac{v_3}{4} \cdot 2$

$2v_g - \frac{4}{3}v_2 = \frac{2}{3}v_2 - v_A$

$4v_A = -2v_1 - v_3$

$v_A = 2v_2 - 2v_g$

$2v_1 + v_3 = -4v_A$

$v_A = 2(v_2 - v_g)$

$2v_3 = -4v_A$

$v_3 = -2v_A = -4v_2 + 4v_g$

$v_3 + 4v_2 = 4v_g$

$v_2 = \frac{4}{3}v_g$


$3v_2 = 4v_g$

$v_2 = \frac{4}{3}v_g$

$v_3 = -\frac{4}{3}v_g$

$v_1 = -\frac{2}{3}v_g$

c)

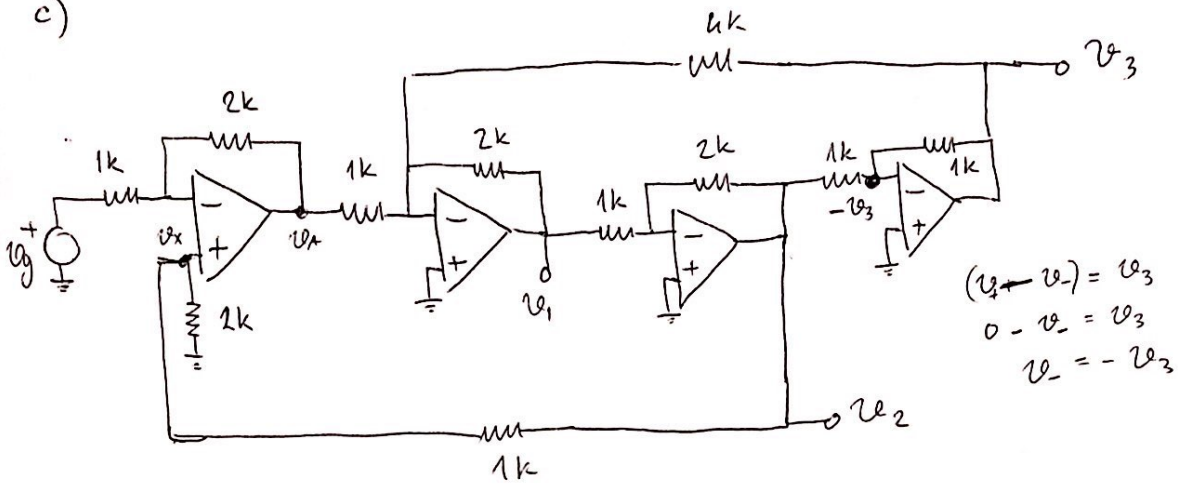

$$\begin{aligned}
 (v_1 + v_3) &= v_3 \\
 0 - v_1 &= v_3 \\
 v_1 &= -v_3
 \end{aligned}$$

$$v_A = \frac{2}{3} v_2$$

$$2v_g - \frac{4}{3}v_2 = \frac{2}{3}v_2 - v_A$$

$$\frac{v_g - \frac{2}{3}v_2}{1} = \frac{\frac{2}{3}v_2 - v_A}{2}$$

$$\boxed{v_A = 2(v_2 - v_g)}$$

$$\frac{v_1}{1} = -\frac{v_2}{2}$$

$$\boxed{v_2 = -2v_1}$$

$$v_2 + v_3 = -2v_3$$

$$\boxed{v_2 = -3v_3}$$

$$\frac{v_A}{1} = \frac{-v_1}{2} - \frac{v_3}{4} \cdot 4$$

$-v_2$

$$-4v_A = 2v_1 + v_3$$

$$-8v_2 + 8v_g = 2v_1 + v_3$$

$$8v_g = 8v_2 + 2v_1 + v_3 = -24v_3 + 3v_3 + v_3$$

$$v_3 = -\frac{8}{20} v_g = -\frac{4}{10} v_g = -\frac{2}{5} v_g = v_3$$


$v_3 = -\frac{2}{5} v_g$
$v_2 = \frac{6}{5} v_g$
$v_1 = -\frac{3}{5} v_g$

$$v_3 = -0,4$$

$$v_2 = 1,2$$

$$v_1 = -0,6$$

Dc:

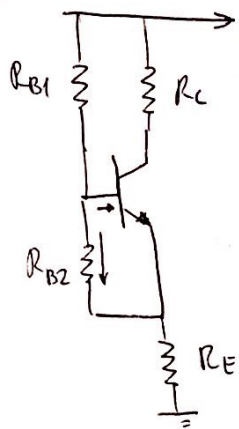

$$V_{CC} - (i_B + i_x) R_{B1} - ((1 + \beta) i_B + i_x) R_E = 0$$

$$V_{CC} - (1 + \beta) i_x R_{B1} - V_{BE} - ((1 + \beta) i_B + i_x) R_E = 0$$

$$i_x = \frac{V_{BE}}{R_{B2}} = 700 \mu A$$


$$V_{CC} - (i_B + i_x) R_{B1} - ((1 + \beta) i_B + i_x) R_E = 0$$

$$V_{CC} - i_B R_{B1} - i_x R_{B1} - (1 + \beta) i_B R_E - i_x R_E = 0$$

$$\frac{V_{CC} - V_{BE} - i_x (R_{B1} + R_E)}{R_{B1} + (1 + \beta) R_E} = i_B = 21,62 \cdot 10^{-5} A = 216,2 \mu A$$

$$V_C = V_{CC} - R_C \cdot \beta \cdot i_B = 7,38 V \quad I_C = 1,31 mA$$
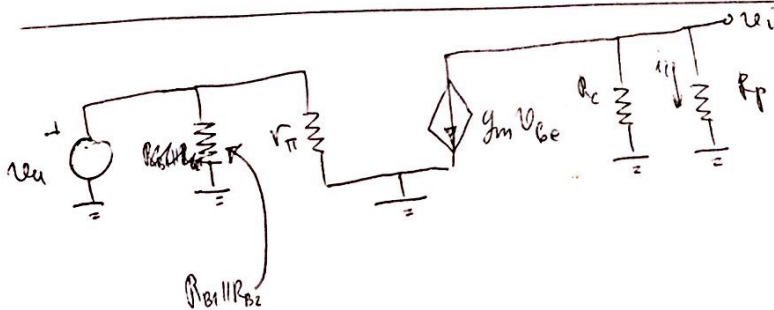
$$g_m = 52,4 mS \quad r_{\pi} = 954,2 \Omega$$



$$i_i = -g_m V_{be} \cdot \frac{R_C}{R_C + R_p}$$

$$i_u = \frac{V_u}{R_{B1} \parallel R_{B2} \parallel r_{\pi}}$$

$$V_i = -g_m V_{be} \cdot R_C \parallel R_p = \underbrace{-g_m R_C \parallel R_p}_{a_v = -52,4} V_u$$

$$\frac{i_i}{i_u} = \frac{-g_m \frac{R_C}{R_C + R_p}}{\frac{1}{R_{B1} \parallel R_{B2} \parallel r_{\pi}}} = \frac{-g_m \cdot R_C \cdot \overbrace{R_{B1} \parallel R_{B2} \parallel r_{\pi}}^{909,1}}{R_C + R_p} = -12,2$$

$$R_{uL} = 465,55 \Omega$$



$$R_{iZL} = 2 k\Omega$$

5

$$V_{eff} = 220V$$

$$V_{max} = 220\sqrt{2}V$$
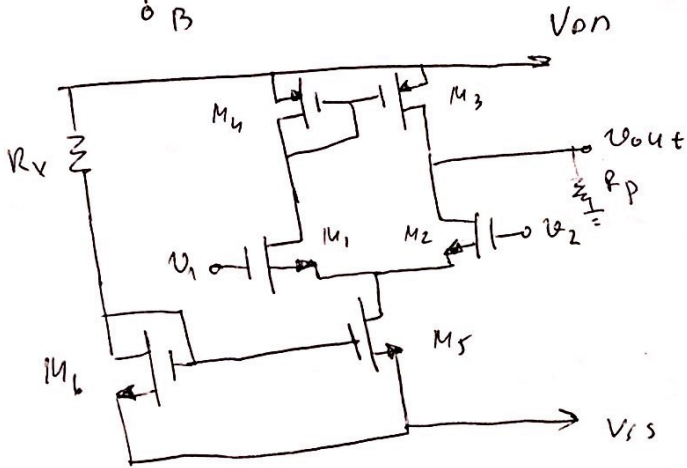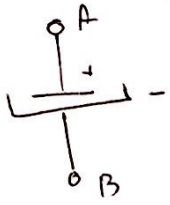
$$\frac{220\sqrt{2}}{20} = R = 11\sqrt{2} = 15.56$$



$$I_{D6} = I_{D5} = 500\mu A$$

$$I_{D4} = I_{D3} = I_{D1} = I_{D2} = 250\mu A$$

$$g_{m5} = g_{m6} = 1mS$$


$$g_{m4} = g_{m3} = g_{m1} = g_{m2} = 0.5mS$$

$$V_{out} = 0V$$

$$I_D = \frac{\beta}{2} (V_{gs} - V_t)^2$$

$$V_g = V_s + \sqrt{\frac{2I_D}{\beta}} + V_t = -3V$$
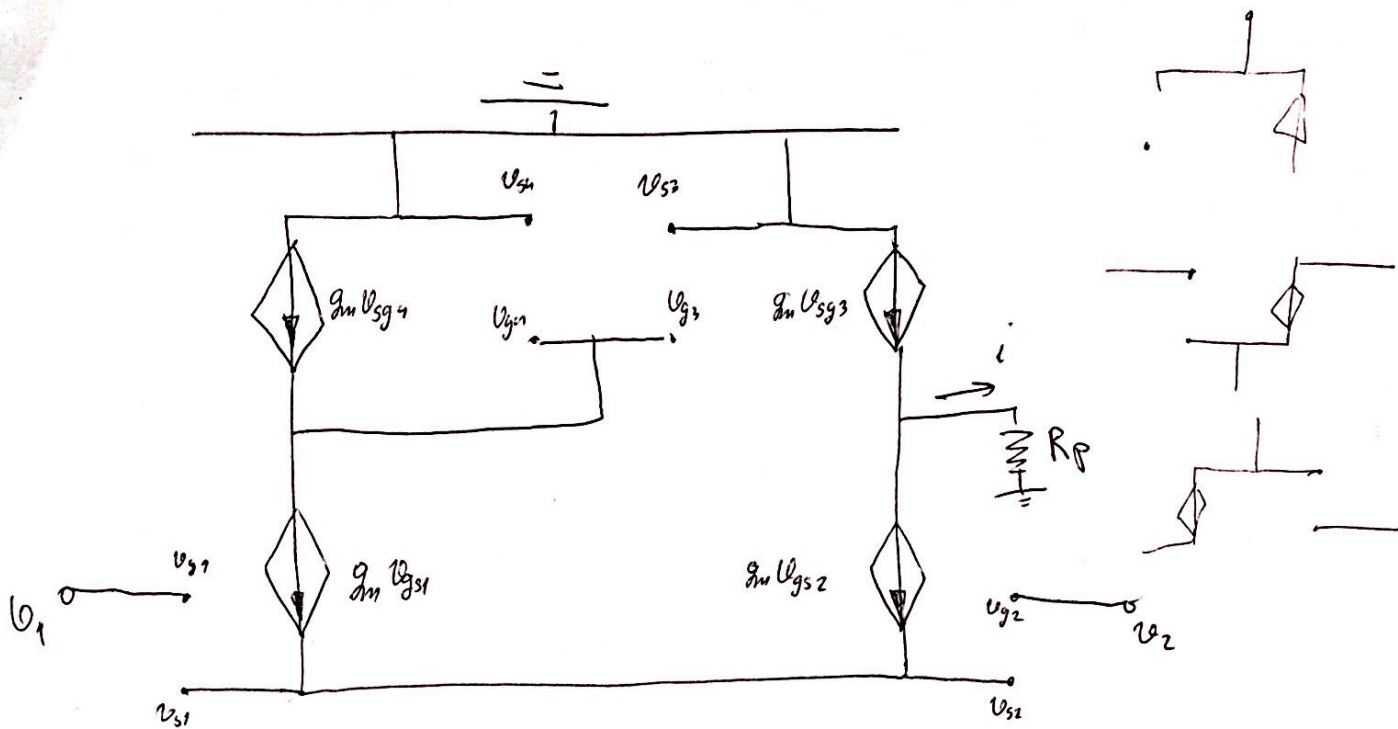
$$\frac{V_{DD} + 3V}{500\mu A} = R_x = 16k\Omega$$



$$g_{m1} v_{gs1} = -g_{m2} v_{gs2}$$

$$g_{m3} v_{sg3} = g_{m2} v_{gs2} + i$$

$$v_1 - v_S = -v_2 + v_S$$

$$i = g_{m3} v_{sg3} - g_{m2} v_{gs2}$$

$$v_1 + v_2 = 2v_S$$

$$v_S = \frac{v_1 + v_2}{2}$$

$$g_{m4} v_{sg4} = g_{m1} v_{gs1} = g_{m3} v_{sg3}$$

$$g_{m4} v_{sg4} = g_{m3} v_{sg3}$$

$$i = g_{m1} v_{gs1} - g_{m2} v_{gs2} =$$

$$= g_{m1} (v_1 - v_S - v_2 + v_S) = g_{m1} v_d \quad v_{out} = g_{m1} \cdot R_p \cdot v_d$$

$$A_d = g_{m1} R_p$$