

$V_2 = 3V$
 $V_B - V_1 = -4$
 $V_B = -1V$


$V_A \left(\frac{1}{2} + \frac{1}{3} \right) - \frac{1}{3} V_1 = -\frac{16}{3} + 1 \quad | \cdot 6$
 $5V_A - 2V_1 = -32 + 6$

$5V_A = -26$
 $V_A = -4V$

- $I_A = 2A$ $P_{3A} = 3W$
- $I_B = 3A$ $P_{3V} = 3W$
- $I_C = 1A$ $P_{16V} = 48W$
- $I_D = 4A$ $P_{1A} = 2W$

$\frac{2 \cdot 3}{5} = \frac{6}{5} + 1 = \frac{11}{5}$

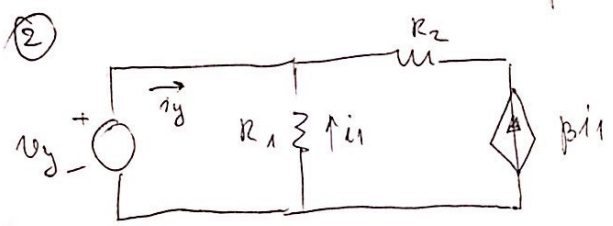$V_T = -3V$ $R_T = \frac{11}{5} \Omega$ $R_p = \frac{11}{5} \Omega$




$i_g = -(1+\beta)i_1$
 $i_1 R_1 + v_g = 0$
 $i_1 = -\frac{v_g}{R_1}$

$A_{EKV} = \frac{R_1}{1+\beta}$

$i_g = \frac{1+\beta}{R_1} v_g$

Jan '19

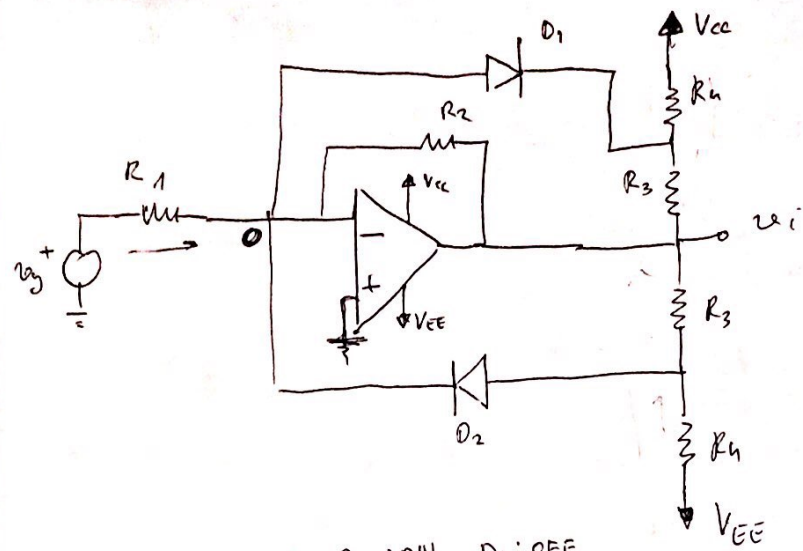

3u $V_g = -3V$ D_2 : ON D_1 : OFF

$$\frac{V_g}{R_1} + \frac{V_i}{R_2} + \frac{V_i}{R_3} - \frac{V_{EE}}{R_4} = 0$$

$$V_i \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = -\frac{V_g}{R_1} - \frac{V_{EE}}{R_4}$$

$$V_i = -\frac{R_2 R_3}{R_1 (R_2 + R_3)} V_g - \frac{R_2 R_3}{(R_2 + R_3) R_4} V_{EE}$$

$$V_i = -2V_g + 2.4$$

$$\frac{V_{cc} - V_x}{R_4} = \frac{V_x - V_i}{R_3}$$


$$\frac{R_3}{R_4} V_{cc} - \frac{R_3}{R_4} V_x = V_x - V_i$$

$$\frac{R_3}{R_4} V_{cc} + V_i = \left(\frac{R_3 + R_4}{R_4} \right) V_x$$

$$V_x = \frac{R_3}{R_4 + R_3} V_{cc} + \frac{R_4}{R_4 + R_3} (-2V_g + 2.4) > 0 \quad D_1 \text{ go OFF}$$

$$i_{D2} = -\frac{V_g}{R_1} - \frac{V_i}{R_2} = -\frac{V_g}{R_1} + \frac{2V_g}{R_2} - \frac{2.4}{R_2} = \text{approx } 90 \mu A$$

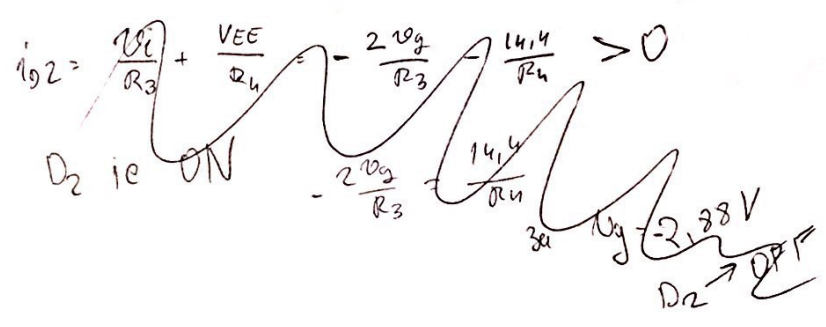~~$V_g = -1.2V$~~ $3u \quad V_g = -1.2V \quad D_2 \rightarrow \text{OFF}$



$$\frac{v_y}{R_1} = -\frac{v_i}{R_2} \quad \boxed{v_i = -4v_y}$$

$$\frac{V_{cc} - v_x}{R_4} = \frac{v_x - v_i}{R_3} \quad v_x = \frac{R_3}{R_3 + R_4} V_{cc} + \frac{R_4}{R_3 + R_4} \cdot (-4v_y) \rightarrow$$

$$\text{so } v_x = 0 \quad \text{inj.} \quad v_y = \frac{R_3}{4R_4} V_{cc} = 1,2 \quad D_1 \rightarrow ON$$

$$\frac{v_y}{R_1} + \frac{V_{cc}}{R_4} + \frac{-v_i}{R_2} + \frac{V_{EE}}{R_3} = 0$$

$$\frac{v_y}{R_1} + \frac{v_i}{R_2} + \frac{V_{cc}}{R_4} = -\frac{v_i}{R_3}$$

$$\frac{2v_i}{R_2} = -\frac{v_y}{R_1} - \frac{V_{cc}}{R_4}$$

$$\boxed{v_i = -2v_y - 2,4}$$

$$\frac{v_y}{R_1} + \frac{v_i}{R_2} = i_D = \frac{4v_y - 2v_y - 2,4}{R_2} = \frac{2v_y - 2,4}{R_2} \rightarrow D_1 \text{ average ON}$$

$$\frac{v_i - v_x}{R_3} = \frac{v_x - V_{EE}}{R_4} \quad \frac{R_4}{R_3} v_i + V_{EE} = v_x \left(\frac{R_3 + R_4}{R_3} \right)$$

$$v_x = \frac{R_4}{R_3 + R_4} v_i + \frac{R_3}{R_3 + R_4} V_{EE} \leq 0$$

4. a) $V_z/R_8=10\text{mA} \rightarrow V_z=5\text{V}$.


b) $V_{\text{out}} = -105\Omega \cdot 10\text{mA} \cdot 10 = -10.5\text{V}$.

c) Kada je temperatura nula na izlazu treba da bude nula, prema tome V_{ref} treba da bude jednako 10V.

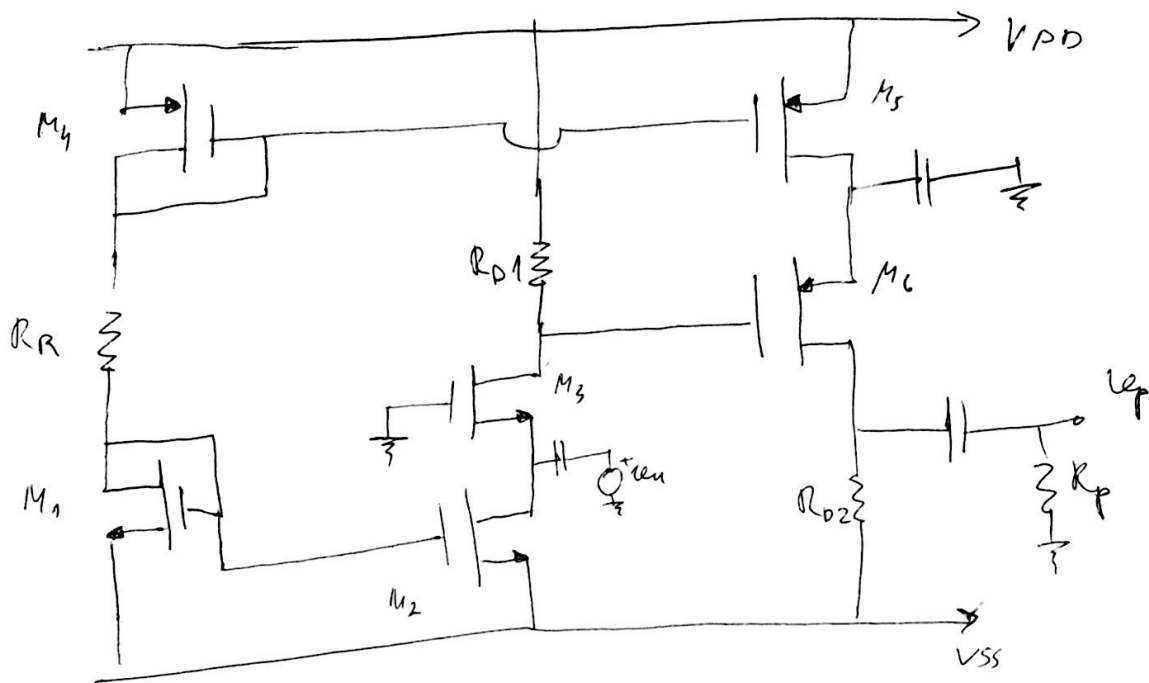d) Minimalni mogući napon na izlazu je -12V.

$$-12\text{V} = -100\text{mV} \cdot T_{\text{max}} / ^\circ\text{C} \rightarrow T_{\text{max}} = 12\text{V} \cdot ^\circ\text{C} / 100\text{mV} = 120^\circ\text{C}$$

$$\text{e) } I = 10\text{mA} - \frac{10\text{mA}}{(1 + \beta)^2} = 10\text{mA} \left(1 - \frac{1}{(1 + \beta)^2} \right)$$



$$I_1 = I_2 = I_3$$

$$R_R = 20 \text{ k}\Omega$$

$$V_{S64} = \sqrt{\frac{2I}{B_4}} + V_t$$

$$V_{G4} = V_{DD} - \sqrt{\frac{2I}{B_4}} - V_t = 10 \text{ V}$$


$$V_{G1} = \sqrt{\frac{2I}{B_1}} + V_t + V_{SS} = -10 \text{ V}$$

$$I_5 = 2 \mu\text{A}$$

$$g_{m3} = 2 \mu\text{S}$$

$$v_{u1} + g_{m7} v_{gs3} R_g = v_{s3}$$

$$g_{m6} = 4 \mu\text{S}$$

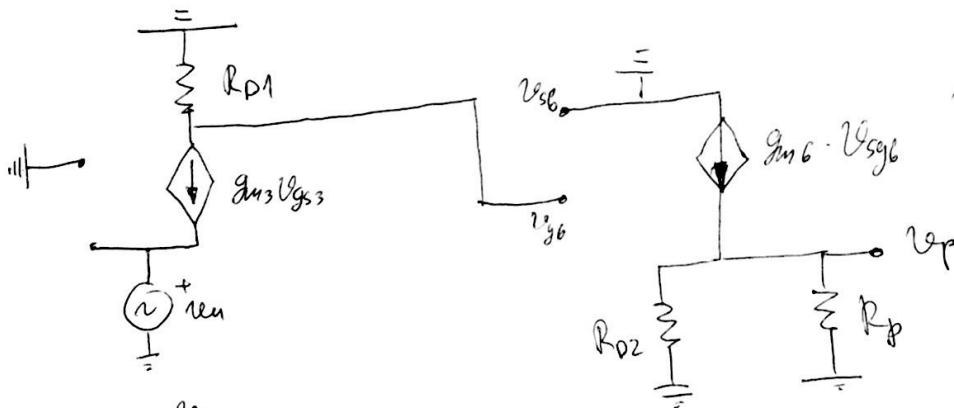

$$v_{s3} = g_{m3} v_{gs3} R_g + v_{u1}$$

$$v_{s3} (1 + g_{m3} R_g) = + v_{u1}$$

$$v_{s3} = + \frac{v_{u1}}{1 + g_{m3} R_g}$$

$$v_{gs3} = - \frac{v_{u1}}{1 + g_{m3} R_g}$$

$$v_{gs3} = -v_{u1}$$

$$v_{sg6} = -g_{m3} \cdot v_{gs3} \cdot R_{D1} = g_{m3} R_{D1} \cdot v_{u1}$$

$$v_p = \frac{-g_{m3} g_{m6} \cdot R_{D1} \cdot R_{D2} \parallel R_p}{a} v_{u1}$$


$$a = -150$$

$$-a_2 = -75$$

$$R_i = R_{D2}$$

$$v_{s3} = g_{m3} v_{gs3} \cdot R_g$$

$$v_{s3} (1 + g_{m3} R_g) = 0$$

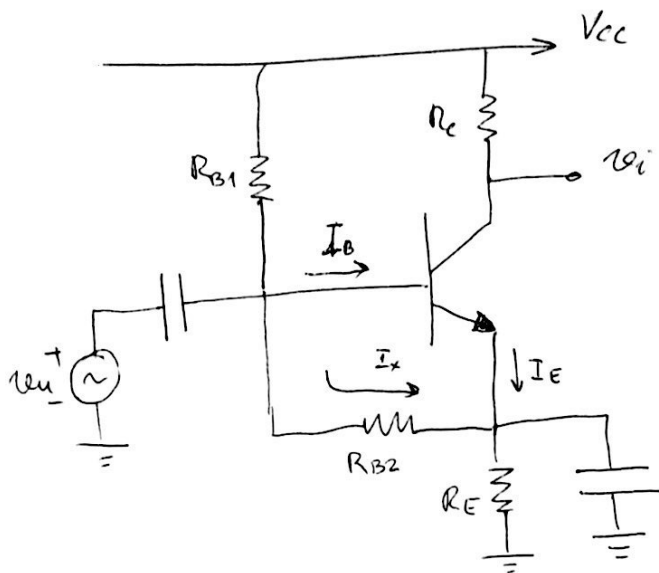

$$I_C = 1.5 \text{ mA}$$

$$I_B = 30 \mu\text{A}$$

$$I_E = 1.53 \text{ mA}$$

$$(I_X + I_E) R_E = V_E \quad V_B = (I_X + I_E) R_E + 0.7$$

$$\frac{V_{BE}}{I_X}$$

$$V_{CC} - R_{B1}(I_B + I_X) = V_B$$


$$V_{CC} - R_{B1}(I_B + I_X) - R_E(I_X + I_E) = 0.7 \text{ V}$$

$$V_{CC} - 0.7 \text{ V} = R_{B1}I_B + \frac{R_{B1}I_X + R_E I_X + R_E I_E}{I_X(R_E + R_{B1})}$$

$$I_X = \frac{2.47}{R_E + R_{B1}} \Rightarrow R_{B2} = \frac{0.7}{I_X} \approx 1031 \Omega$$

$$g_m = 60 \text{ mS} \quad r_{\pi} = 833.33 \Omega$$

$$R_{B1} \parallel R_{B2} =$$

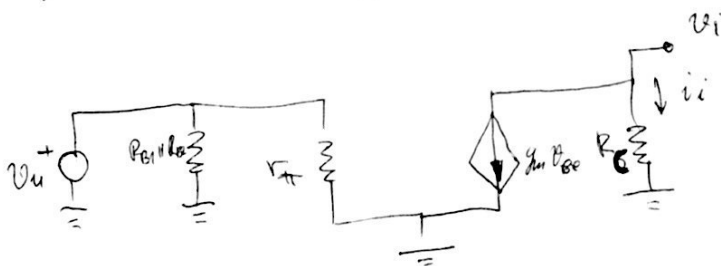

$$v_i = i_i \cdot R_c = - \frac{\beta R_c}{r_{\pi}} \cdot v_u =$$

$$a_v = -120$$




$$a_v = -50$$

$$i_b = \frac{v_u}{r_{\pi}}$$


$$i_i = -\beta i_b = - \frac{\beta \cdot v_u}{r_{\pi}}$$


$$v_u = \frac{v_{in}}{r_{\pi} \parallel R_{B1} \parallel R_{B2}}$$
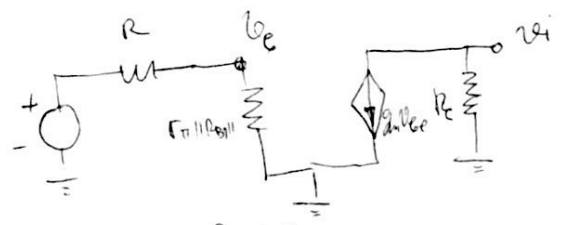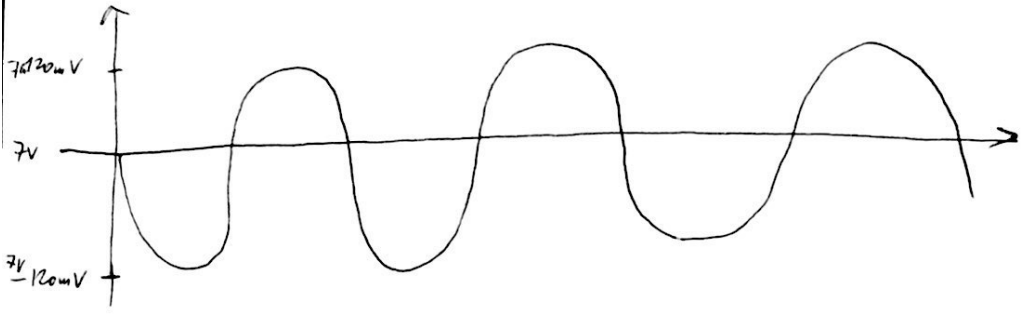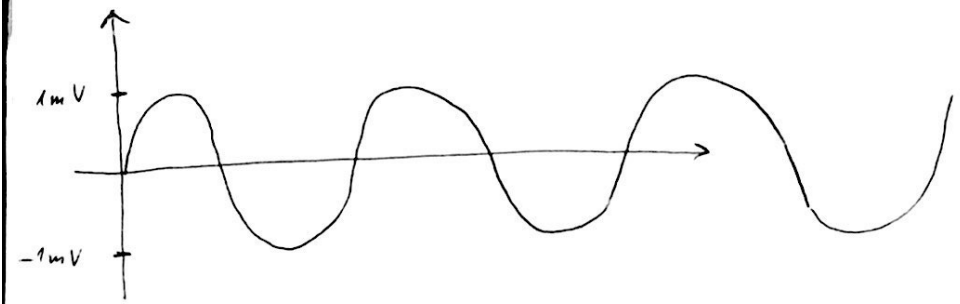
$$v_i = \frac{-\beta \cdot r_{\pi} \parallel R_{B1} \parallel R_{B2}}{r_{\pi} \cdot R_c} = -261.42$$


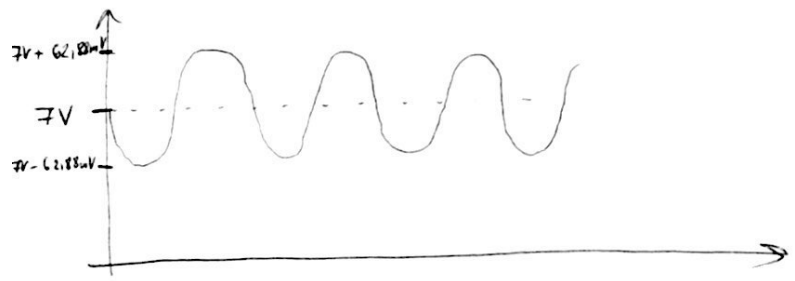
$$V_b = \frac{r_{\pi} \parallel R_{B1} \parallel R_{B2}}{R + r_{\pi} \parallel R_{B1} \parallel R_{B2}} V_g \Rightarrow V_i = -g_m V_b \cdot R_c = \underbrace{-62,88}_a V_g$$



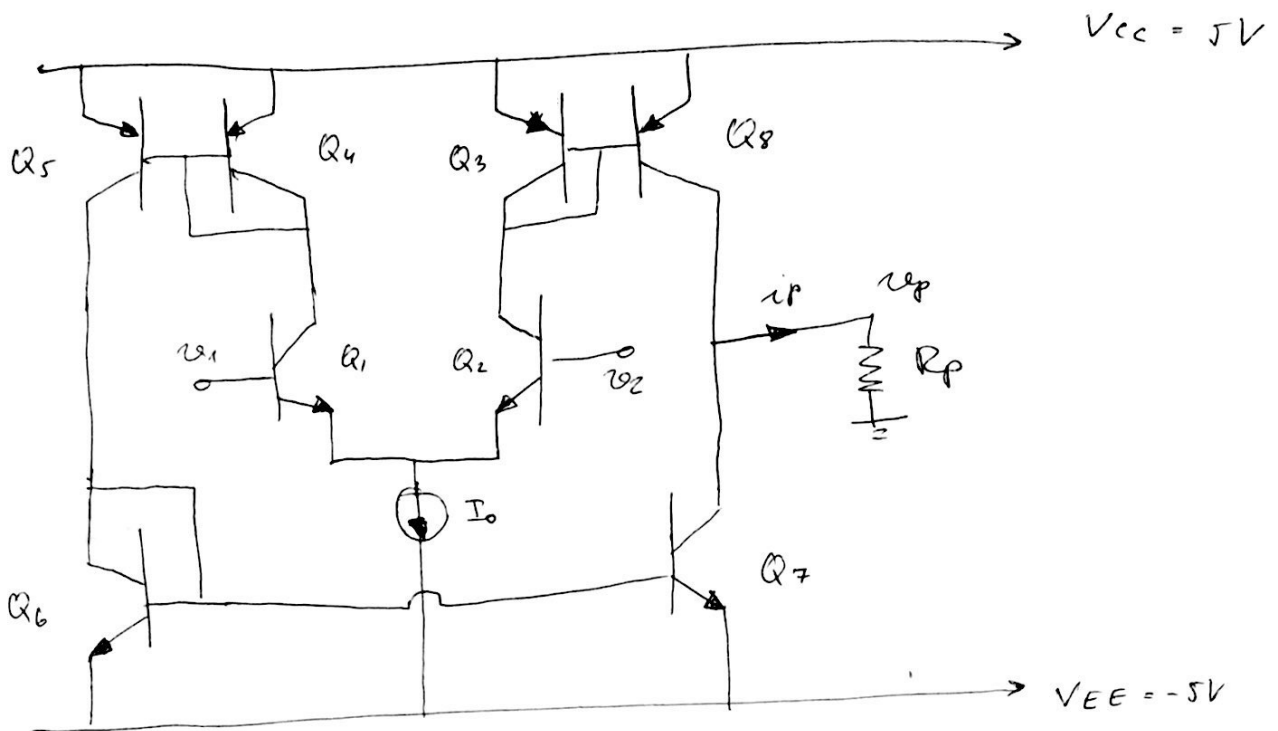

$$I_{E1} = I_{E2} = \frac{I_o}{2} = 100 \mu A$$

$$I_{C1} = I_{C2} = 99,01 \mu A$$

$$I_{C4} + 2I_{B4} = I_{C1}$$

$$I_{B4} = \frac{I_{C1}}{2 + \beta} = 0,9706 \mu A$$

$$I_{C4} = 97,06 \mu A = I_{C5} = I_{C8}$$


$$I_{C6} + 2I_{B6} = I_{C5}$$

$$I_{B6} = \frac{I_{C5}}{\beta + 2} = 0,952 \mu A$$

$$I_{C6} = 95,2 \mu A$$

$V_p = 18,6 \mu V$
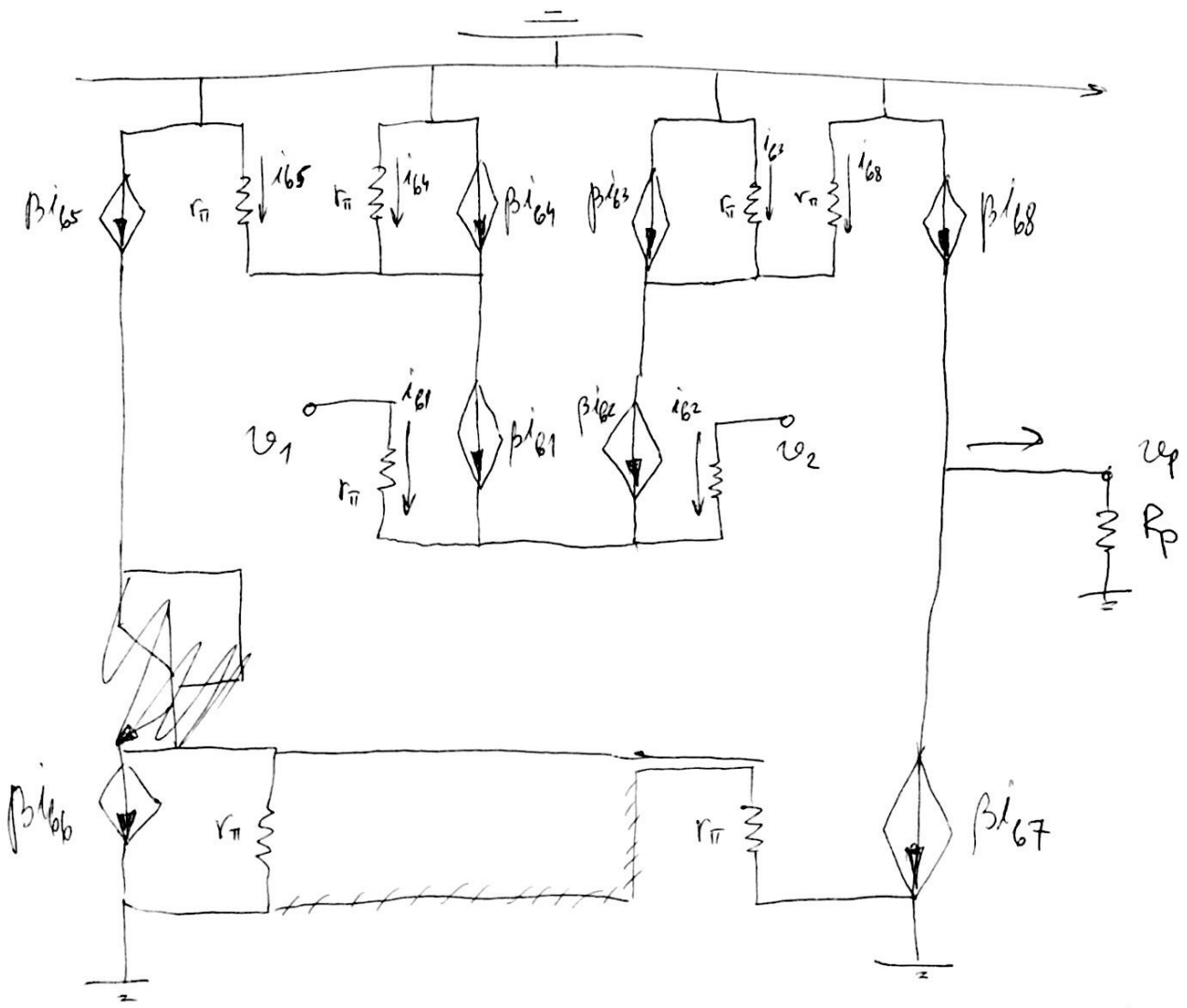
$$g_m = 4 mS \quad r_{\pi} = 25 k\Omega$$



$$i_{D1} = \frac{v_1 - v_2}{2r_{\pi}} \quad i_{D2} = \frac{v_2 - v_1}{2r_{\pi}}$$

$$v_{g1} = 1mV \cos \omega t$$

$$v_{g2} = -2mV \cos \left(\omega t + \frac{\pi}{6} \right)$$

$$i_{D7} = i_{D1}$$

$$i_{D8} = i_{D2}$$

$$i_p = 2\beta i_{D2}$$

$$v_{g2} = -\sqrt{2} \left(\frac{\sqrt{3}}{2} + \frac{1}{2}j \right)$$

$$= -\frac{\sqrt{2}}{2} (\sqrt{3} + j)$$


$$v_p = -\frac{\beta R_P}{r_{\pi}} \cdot v_d \Rightarrow \boxed{a = -0,04}$$

$$\sqrt{2} \left(\frac{\sqrt{3}}{2} + \frac{1}{2}j \right)$$

$$v_p = -0,04 \left(1mV \cos \omega t + 2mV \cos \left(\omega t + \frac{\pi}{6} \right) \right)$$

$$v_{g1} = \frac{\sqrt{2}}{2} mV \quad v_{g2} = -\left(\frac{\sqrt{6}}{2} + \frac{\sqrt{2}}{2}j \right) = -\frac{\sqrt{2}}{2} (\sqrt{3} + j)$$
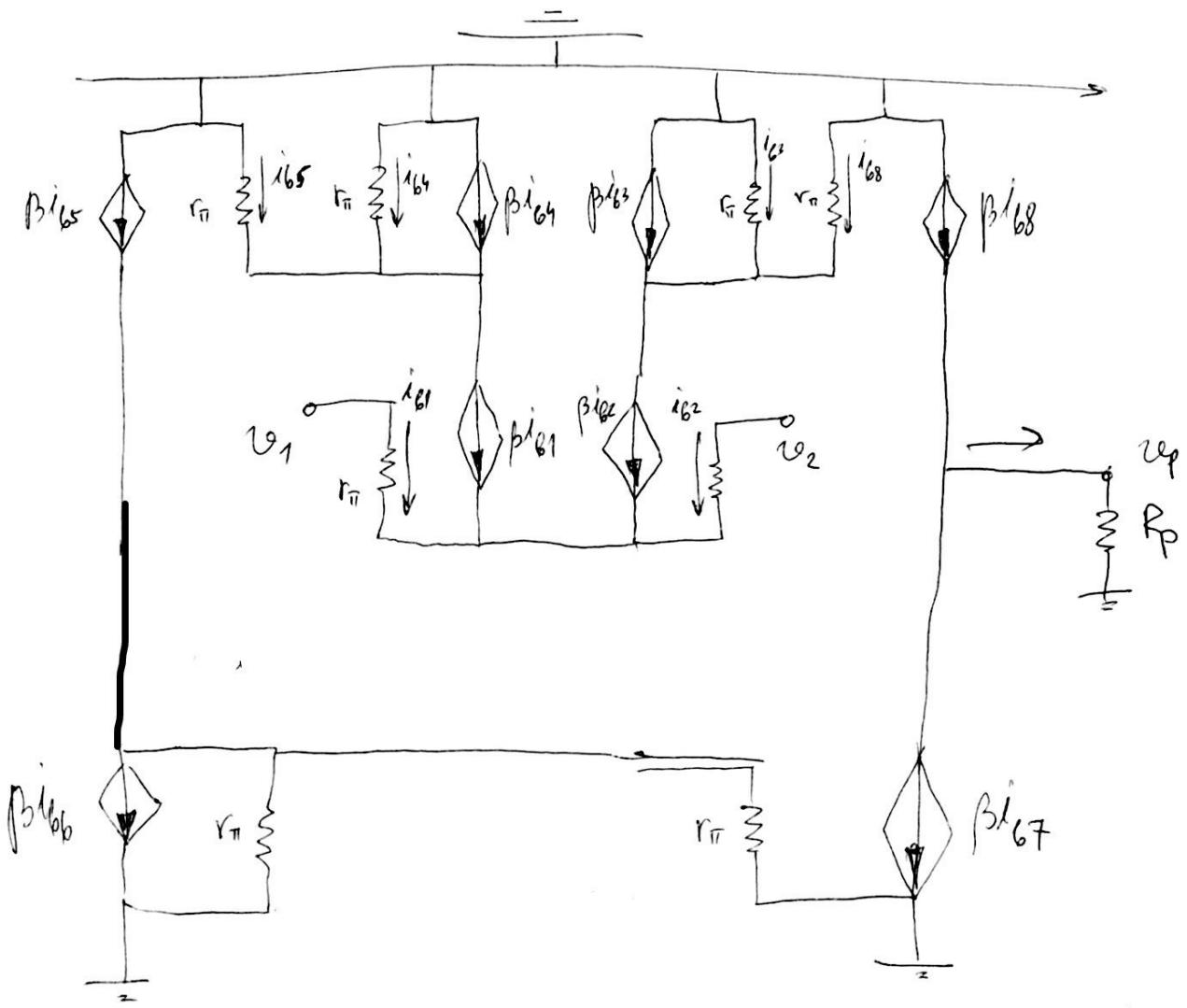
$$v_{g1} - v_{g2} = \frac{\sqrt{2}}{2} (1 + \sqrt{3} + j)$$



$$i_{b1} = \frac{v_1 - v_2}{2r_{\pi}} \quad i_{b2} = \frac{v_2 - v_1}{2r_{\pi}}$$

$$v_{g1} = 1 \text{ mV} \cos \omega t$$

$$v_{g2} = -2 \text{ mV} \cos \left(\omega t + \frac{\pi}{6} \right)$$

$$i_{b7} = i_{b1}$$

$$i_{b8} = i_{b2}$$

$$i_p = 2\beta i_{b2}$$

$$v_{g2} = -\sqrt{2} \left(\frac{\sqrt{3}}{2} + \frac{1}{2}j \right)$$

$$= -\frac{\sqrt{2}}{2} (\sqrt{3} + j)$$

$$v_p = -\frac{\beta R_P}{r_{\pi}} \cdot v_d \Rightarrow \boxed{a = -0,04}$$

$$\sqrt{2} \left(\frac{\sqrt{3}}{2} + \frac{1}{2}j \right)$$

$$v_p = -0,04 \left(1 \text{ mV} \cos \omega t + 2 \text{ mV} \cos \left(\omega t + \frac{\pi}{6} \right) \right)$$

$$v_{g1} = \frac{\sqrt{2}}{2} \text{ mV} \quad v_{g2} = -\left(\frac{\sqrt{6}}{4} + \frac{\sqrt{2}}{4}j \right) = -\frac{\sqrt{2}}{2} (\sqrt{3} + j)$$

$$v_{g1} - v_{g2} = \frac{\sqrt{2}}{2} (1 + \sqrt{3} + j)$$