

jan '19

① a)  $3R \parallel 6R = \frac{18R^2}{9R} = 2R$

$V_T = -2R(I_{G1} + I_{G2})$



$V_{AB} = -2R(I_{G1} + I_{G2})$

$R_T = 2R$

$P_{IG1} = 2R I_G (I_{G1} + I_{G2})$      $P_{SR} = 0W$

$R_p = 2R$

D: ON, DZ: *napredoj*

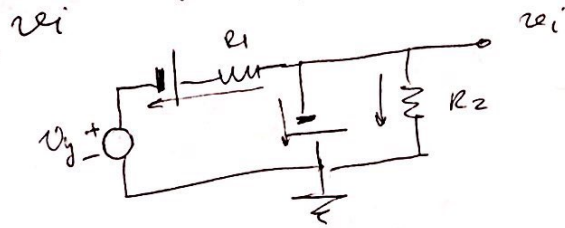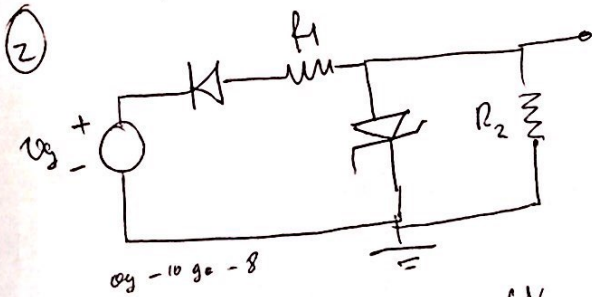


$V_i = -6V$      $i_{R2} = -\frac{6V}{3k\Omega} = -2\mu A$

$i_{R2} \cdot R_2 = i_D R_1 - V_g - V_D = 0$      $-6.7 - i_D R_1 - V_g = 0$

$i_D = -\frac{V_g + 6.7V}{R_1}$      $i_Z = -(i_D + i_{R2}) = \frac{V_g + 6.7V}{R_1} + 2\mu A = 10\mu A + 8.7\mu A$

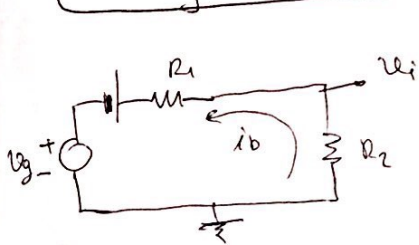3a  $V_g = -8.7V$  DZ  $\rightarrow$  OFF




$V_g + V_D + i_D(R_1 + R_2)$

$i_D = -\frac{1}{4} V_g - 0.175 > 0$

3a  $V_g = -0.7V$  D  $\rightarrow$  OFF

$V_i = \frac{3}{4} V_g + 0.1525$      $2^\circ$   
 $V_g = -8V$      $g = -0.7V$

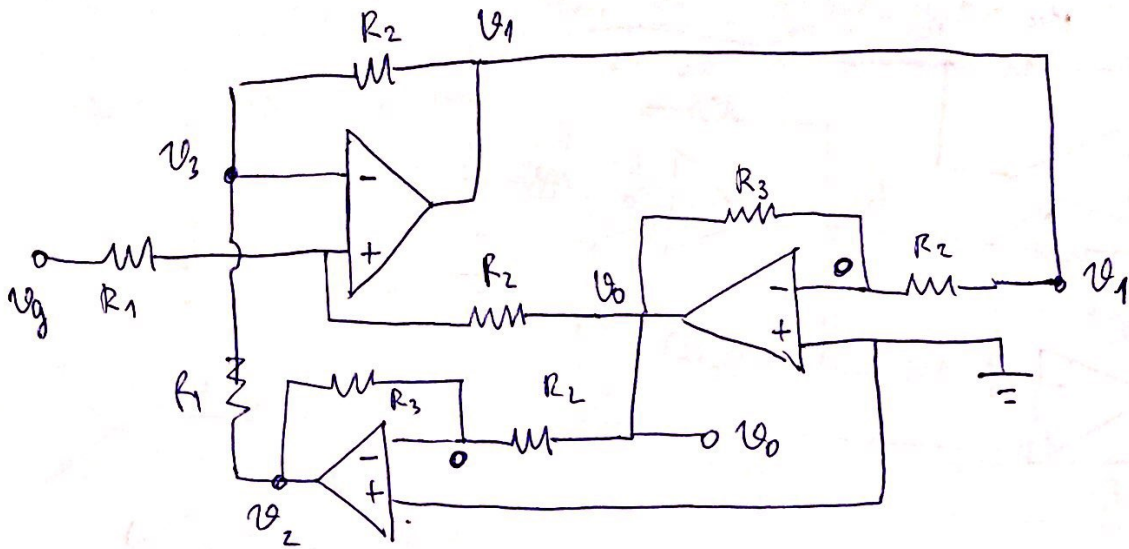$V_i = 0V$      $3^\circ$      $V_g = -0.7V$  or  $10V$



$$\frac{v_0}{R_3} = -\frac{v_1}{R_2} \quad \boxed{v_1 = -\frac{2}{3}v_0}$$

$$\frac{v_0}{R_2} = -\frac{v_2}{R_3} \quad \boxed{v_2 = -\frac{3}{2}v_0}$$

$$\frac{v_2 - v_3}{R_1} = \frac{v_3 - v_1}{R_2} \quad 2v_2 - 2v_3 = v_3 - v_1$$

$$3v_3 = 2v_2 + v_1 \quad v_3 = \frac{2}{3}v_2 + \frac{1}{3}v_1$$

$$v_3 = -v_0 - \frac{2}{9}v_0 = -\frac{11}{9}v_0$$


$$\frac{v_g - v_3}{R_1} = \frac{v_3 - v_0}{R_2} \quad 2v_g - 2v_3 = v_3 - v_0$$

$$v_0 = 3v_3 - 2v_g = -\frac{11}{3}v_0 - 2v_g$$

$$\frac{14v_0}{3} = -2v_g \quad \boxed{v_0 = -\frac{3}{7}v_g}$$

a)  $\bar{u}$ : Q: OFF, DZ: OFF  $V_e = 1V$   
 $V_{b2} = -1V$   $V_{b0} = 0V$

b)  $\bar{u}$ : Q: gain, DZ: not needed

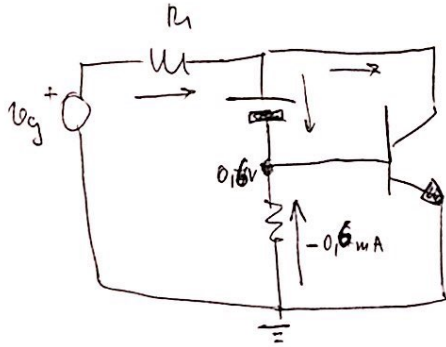

$V_c = 3V$

$0.6 + 3V + iR_1 = V_g = 0$

$i = \frac{8 - 3V}{R_1} = 2.125mA$

$2.12mA = (1 + \beta)i_c + 0.6mA$

$2.105mA = (1 + \beta)i_c + 0.6mA$


$i_c = -0.1614mA$

$V_g = -\frac{R_s}{R_{in}} \cdot V_i$

$V_{gs} = V_g + \frac{R_s}{R_s} V_i$

$V_s - V_i = -(1 + \frac{R_s}{R_F}) V_i$

in  $V_{gs}$

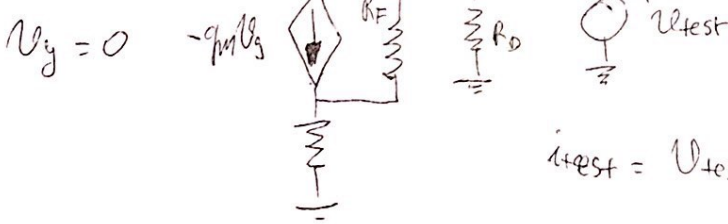

$i_{test} = \frac{V_{test}}{R_D} - g_m V_s + \frac{V_{test} - V_s}{R_F}$

$i_{test} = V_{test} \left( \frac{1}{R_D} + \frac{-g_m + g_m R_F + \frac{R_F}{R_s}}{\frac{R_F}{R_s} + g_m R_F + 1} \right)$


$-g_m V_s + \frac{V_{test} - V_s}{R_F} = \frac{V_s}{R_s}$

$\frac{V_{test}}{R_F} = V_s \left( \frac{1}{R_s} + \frac{1}{R_F} + g_m \right)$

$V_{test} = V_s \left( \frac{R_F}{R_s} + g_m R_F + 1 \right)$

$V_s = \frac{V_{test}}{\frac{R_F}{R_s} + g_m R_F + 1}$   $V_{test} - V_s = V_{test} \left( 1 - \frac{1}{\frac{R_F}{R_s} + g_m R_F + 1} \right) = V_{test} \cdot \frac{\frac{R_F}{R_s} + g_m R_F}{1 + g_m R_F + \frac{R_F}{R_s}}$

DC:

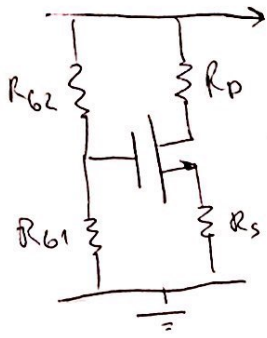

$$\frac{R_{01}}{R_{01} + R_{62}} V_{DD} = 4V$$

$$V_G = 4V$$

$$V_S = I_D R_S$$

$$500^2 I_D^2 - 5000 I_D + 9 = 0$$

$$I_{D1/2} = \frac{5000 \pm 4000}{2 \cdot 500^2}$$




~~$$I_{D1} = 18 \mu A \quad V_{S1} = 9V \quad V_{D1}$$~~

$$I_{D2} = 2 \mu A \quad V_{S2} = 1V$$

$$I_D = \frac{\beta}{2} (V_G - I_D R_S - V_t)^2$$

$$2000 I_D = (3 - 500 I_D)^2$$

$$V_i = V_{DD} - R_D I_D = 12 - 4 = 8V$$

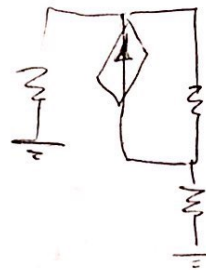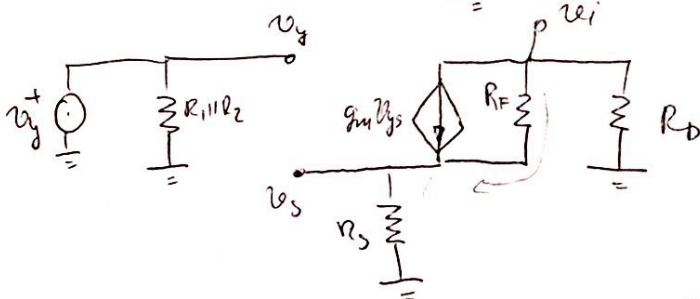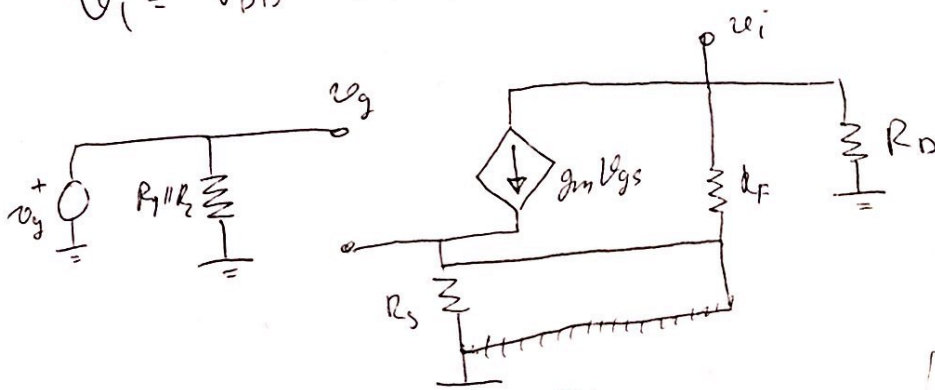


$$g_m v_{gs} + \frac{v_i - v_s}{R_F} - \frac{v_s}{R_S} = 0 \quad -g_m v_{gs} - \frac{v_i - v_s}{R_F} - \frac{v_i}{R_D} = 0$$

$$\frac{v_i - v_s}{R_F} - \frac{v_s}{R_S} - \frac{v_i - v_s}{R_F} - \frac{v_i}{R_D} = 0$$

$$v_s = - \frac{R_S}{R_D} v_i$$

$$\frac{v_i - v_s - v_i + v_s}{R_F} - \frac{v_s}{R_S} - \frac{v_i}{R_D} = 0$$

$$v_{gs} = v_g + \frac{R_S}{R_D} v_i$$

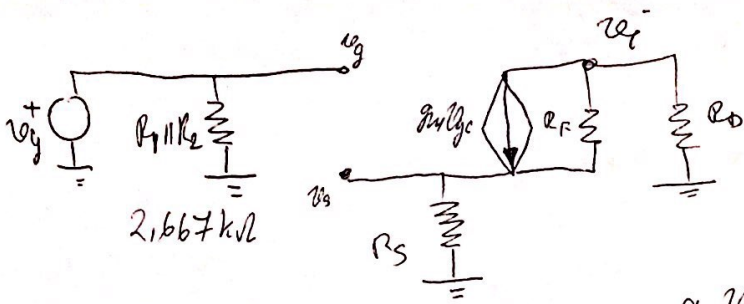

$$g_m V_{gs} + \frac{V_i - V_s}{R_F} - \frac{V_s}{R_S} = 0$$

$$\frac{V_i - V_s}{R_F} + g_m V_{gs} = \frac{V_s}{R_S}$$

$$-g_m V_{gs} + \frac{V_s - V_i}{R_F} - \frac{V_i}{R_D} = 0$$

$$-\frac{V_i}{R_D} = \frac{V_s}{R_S}$$

$$V_i = -\frac{R_D}{R_S} V_s$$

$$\frac{V_s (R_S + R_D)}{R_S R_F} = -\frac{V_s \frac{R_D}{R_S}}{R_D} + g_m V_g - g_m V_s$$

$$V_s \cdot \frac{R_S + R_D}{R_S R_F} + V_s \frac{1}{R_S} + g_m V_s = g_m V_g$$

$$V_s \left( \frac{R_S + R_D}{R_S R_F} + \frac{1}{R_S} + g_m \right) = g_m V_g$$

$$V_s = \frac{g_m}{\frac{R_S + R_D}{R_S R_F} + \frac{1}{R_S} + g_m} V_g$$

$$V_i = \frac{-R_D g_m}{R_S \cdot \frac{R_S}{R_S R_F} + R_S \cdot \frac{R_D}{R_S R_F} + \frac{R_S}{R_S} + g_m R_S} V_g$$

$$= - \frac{g_m}{\frac{R_S}{R_D R_F} + \frac{1}{R_F} + \frac{1}{R_D} + g_m \frac{R_S}{R_D}} V_g$$

$$a = -1.231$$

$$V_s = - \frac{R_s}{R_D} \cdot V_i$$


$$+g_m \quad \underbrace{V_{gs} = V_g + \frac{R_s}{R_D} V_i}$$

$$V_s - V_i = - \left(1 + \frac{R_s}{R_D}\right) V_i$$

$g_m V_{gs} =$

$$V_g = 0$$

$$-g_m V_s$$

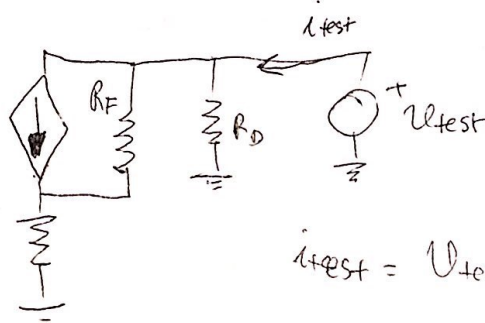

$$i_{test} = \frac{V_{test}}{R_D} - g_m V_s + \frac{V_{test} - V_s}{R_F}$$

$$i_{test} = V_{test} \left( \frac{1}{R_D} + \frac{-g_m + g_m R_F + \frac{R_F}{R_s}}{\frac{R_F}{R_s} + g_m R_F + 1} \right)$$

$R_{iZL}^{-1}$


$$-g_m V_s + \frac{V_{test} - V_s}{R_F} = \frac{V_s}{R_s}$$

$$\frac{V_{test}}{R_F} = V_s \left( \frac{1}{R_s} + \frac{1}{R_F} + g_m \right)$$

$$V_{test} = V_s \left( \frac{R_F}{R_s} + g_m R_F + 1 \right)$$

$$V_s = \frac{V_{test}}{\frac{R_F}{R_s} + g_m R_F + 1}$$
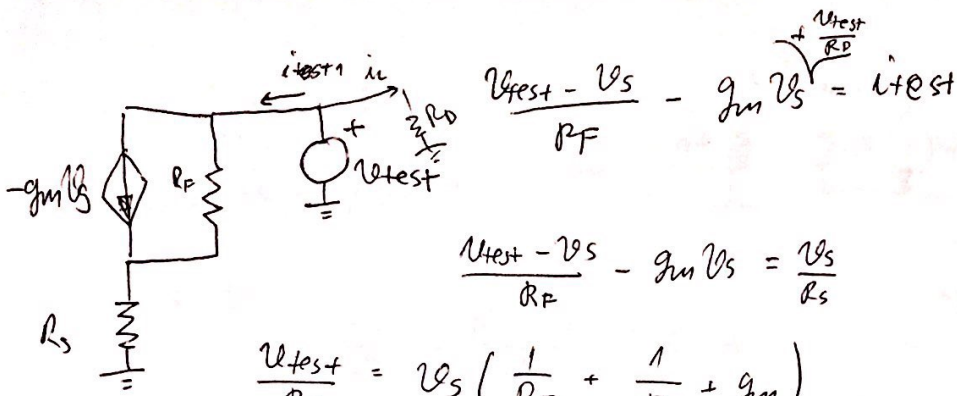
$$V_{test} - V_s = V_{test} \left( 1 - \frac{1}{\frac{R_F}{R_s} + g_m R_F + 1} \right) = V_{test} \cdot \frac{\frac{R_F}{R_s} + g_m R_F}{1 + g_m R_F + \frac{R_F}{R_s}}$$



$$\frac{v_{test} - v_s}{R_F} - g_m v_s = i_{test}$$

$$\frac{v_{test} - v_s}{R_F} - g_m v_s = \frac{v_s}{R_S}$$

$$\frac{v_{test}}{R_F} = v_s \left( \frac{1}{R_F} + \frac{1}{R_S} + g_m \right)$$

$$v_{test} = v_s \left( 1 + \frac{R_F}{R_S} + g_m R_F \right)$$

$$v_s = \frac{v_{test}}{1 + g_m R_F + \frac{R_F}{R_S}}$$

$$v_{test} = v_{oc} = \frac{v_{test} \left( 1 - \frac{1}{1 + g_m R_F + \frac{R_F}{R_S}} \right) - \frac{g_m v_{oc} R_F}{1 + g_m R_F + \frac{R_F}{R_S}}}{R_F}$$

$$v_{test} \left( \frac{1}{R_D} + \frac{g_m R_F + \frac{R_F}{R_S} - g_m R_F}{R_F \left( 1 + g_m R_F + \frac{R_F}{R_S} \right)} \right) = i_{test}$$

$$R_{iZL} = \left( \frac{1}{R_D} + R_S \left( 1 + g_m R_F + \frac{R_F}{R_S} \right) \right)^{-1} = \left( R_F + R_S + g_m R_F R_S \right) \parallel R_D = 1138 \Omega$$

$$R_{iZL} = 1138 \Omega = R_{iZL}$$