

74) $V_{\gamma} = V_{BE} = 0.6V$ $V_{BES} = 0.6V$ $V_{CES} = 0.2V$ $\beta = 100$ $V_{CC} = 12V$ $R_1 = 10k\Omega$ $R_2 = 1k\Omega$


н.н. Q - OFF

$i_B = i_C = i_E = 0$ $V_E = 0$ $V_{BE} = 0 < V_{\gamma} \Rightarrow Q \text{ OFF}$ (T)

75) ~~V_{CE} > V_{CES}~~

Q → gap

~~$V_{CE} > V_{CES}$~~

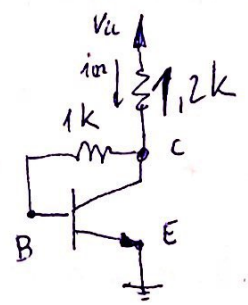

$i_C + i_B = i_E$

$V_{CC} - i_{R2} \cdot R_2 - i_B \cdot R_1 - V_{BE} = 0$

$i_{R2} = i_C + i_B = i_E$

$V_{CC} - \beta \cdot i_B \cdot R_2 - i_B R_1 - V_{BE} = 0$

$(1 + \beta) i_B R_2 + i_B R_1 = V_{CC} - V_{BE}$

$\frac{V_{CC} - V_{CE}}{R_2} = i_{R2}$ $V_{CE} = V_{CC} - R_2 i_{R2}$

$i_B = \frac{V_{CC} - V_{BE}}{(1 + \beta) R_2 + R_1}$

$V_{CE} = V_C - 0 = V_{CC} - R_2 i_{R2} = V_{CC} - R_2 (1 + \beta) i_B = 1.18V$


$i_E = i_B + i_C$ $i_C = \beta \cdot i_B$

Q je y gap-y $> V_{CES}$

$V_B = V_{BE} = 0.7V$

$V_E = 0$

76

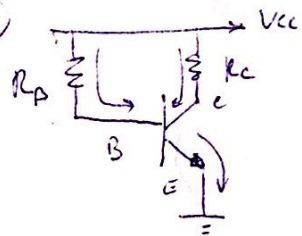

$V_E = 0$ н.н. gap

$V_{CE} > V_{CES}?$

$V_{CE} = V_{CC} - i_C R_C = V_{CC} - \beta \cdot i_B R_C$

~~$V_{CC} - i_C R_C = V_{CE} = 0$~~

$V_{CE} = V_{CC} - \beta \cdot R_C \cdot \frac{V_{CC} - V_{BE}}{R_B} = 1.17V < V_{CES}$

$V_{CC} - i_B R_B - V_{BE} = 0$

$i_B = \frac{V_{CC} - V_{BE}}{R_B}$

(T) Hnje gap

н.н. zac

$V_{BE} = V_{BES}$ $V_{CE} = V_{CES}$

$\beta i_B > i_C?$

$V_B = V_{BES}$ $V_C = V_{CES}$
 $V_E = 0$


$\beta \cdot i_B = \beta \cdot \frac{V_{CC} - V_{BES}}{R_B} = 12mA$

$\beta i_B > i_C$

$i_B = 120\mu A$ $i_C = 280\mu A$

$i_C = \frac{V_{CC} - V_{CES}}{R_C} = 0.28mA$


$i_E = i_B + i_C = 400\mu A$

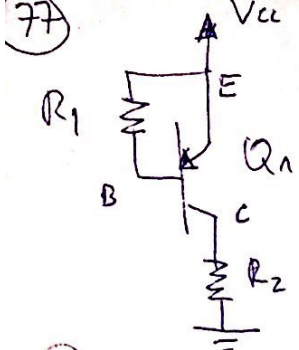

Q: gar zak $V_{EB} < V_{\gamma}$ $V_{EB} = 0 < V_{\gamma}$ (T)

$V_{EB} > V_{EBS}$? $V_E = V_{CC}$ $V_B = V_{CC}$

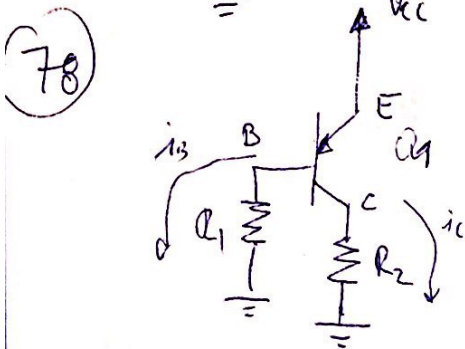$V_E = V_{CC}$ $V_C = 0$ $i_C = 0, i_B = 0, i_E = 0$



Q: gar (T)

$V_{EC} > V_{ECS}$ $V_E = V_{CC}$

$V_C = +i_C R_2 = +\beta R_2 \cdot i_B$

$V_{EC} = V_{CC}$ $V_{CC} - V_{EB} - I_B R_1 = 0$

$I_B = \frac{V_{CC} - V_{EB}}{R_1} = 57 \mu A$


$V_{EC} = V_{CC} = \beta \cdot R_2 \cdot \frac{V_{CC} - V_{EB}}{R_1} = 6,3 V > V_{ECS}$

$i_C = \beta i_B = 5,7 mA$ $i_E = 5,757 mA$

$V_E = V_{CC}$

$V_B = V_E - V_{EB}$

$V_C = V_{EC} - V_{EC}$

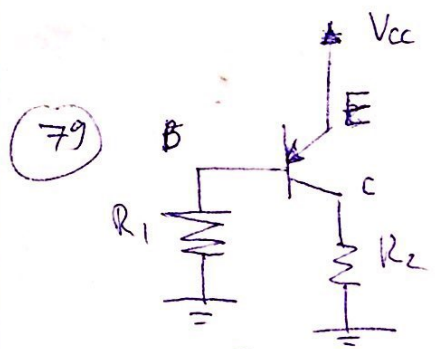

Q: zak:

$V_E = V_{CC}$ $V_B = 0$ $V_C = 0$

$V_{EB} < V_{\gamma}$ (L)

$V_{EC} > V_{\gamma}$

Q: gar (L)

$V_{EB} = V_{EB}$

$V_{EC} > V_{ECS}$

$V_E = V_{CC} = 12V$

Q: zak $\beta I_B \neq i_C$?

$V_B = V_{EBS}$ $V_E - V_B = V_{EB}$ $V_B = V_E - V_{EBS} = 11,4V$

$V_{EC} = V_{ECS}$ $V_E - V_C = V_{EC}$ $V_C = \frac{V_E - V_{EC}}{\beta} = 11,8V$

$\beta I_B = \beta \frac{V_{CC} - V_{EBS}}{R_1} = 11,2 \mu A$ $I_B = 11,2 \mu A$

$i_C = \frac{V_{CC} - V_{ECS}}{R_2} = 11,9 \mu A$ $I_E = 12,9 \mu A$


$V_{CC} - V_{EC} - i_C R_2 = 0$

$V_{EC} = V_{CC} - i_C R_2 = V_{CC} - \beta R_2 \cdot \frac{V_{CC} - V_{EB}}{R_1} = -102 V < V_{ECS}$

$i_C = \beta i_B$

$V_{CC} - V_{EB} - I_B R_1 = 0$

$I_B = \frac{V_{CC} - V_{EB}}{R_1}$

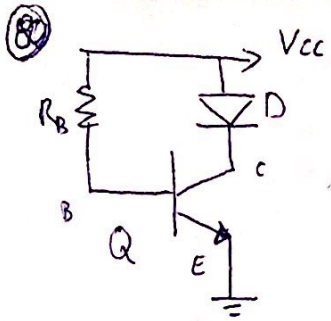

Q - OFF u D OFF

$$i_B = i_C = i_E = 0$$

$$V_B = V_{CC}$$

$$V_{BE} < V_{\gamma}$$

$$V_{CC} < V_{\gamma} \quad \perp$$

36

Q ON u D ON

$$V_{CE} > V_{CES} ?$$

$$i_D > 0 ? \quad i_D = i_C$$

$$V_C = V_{CC} - V_D \quad V_{CE} = V_{CC} - V_D > V_{CES} \quad \perp$$

$$V_E = 0$$

$$V_{BE} = V_{BE} \quad V_B = V_{BE}$$


$$i_B = \frac{V_{CC} - V_{BE}}{R_B} = 120 \mu A$$

$$i_C = \beta i_B = 12 mA > 0$$

$$i_E = 12,12 mA$$

$$V_B = 0,7 V$$

81

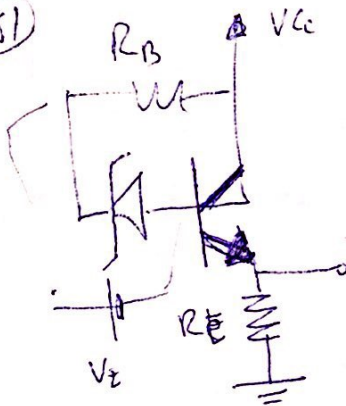

$$V_C = V_{CC}$$

in: gap

02: wprost

$$V_{CE} > V_{CES} ?$$

$$V_C = V_{CC}$$

$$V_{CC} - i_B R_B - V_Z - V_{BE} - (1 + \beta) i_B R_E = 0$$

$$\frac{V_{CC} - V_Z - V_{BE}}{R_B + (1 + \beta) R_E} = i_B = 308,5 \mu A$$

$$R_B + (1 + \beta) R_E$$

$$I_D < 0$$



$$V_E = V_Z = (1 + \beta) i_B \cdot R_E = 3,12 V$$

$$V_{CE} = V_{CC} - (1 + \beta) i_B R_E = 6,88 V > V_{CES}$$

8)


$$V_{CC} = V_Z + V_{BE}$$

82

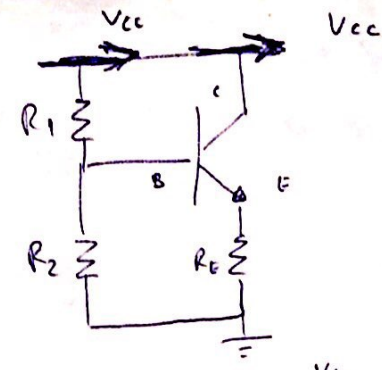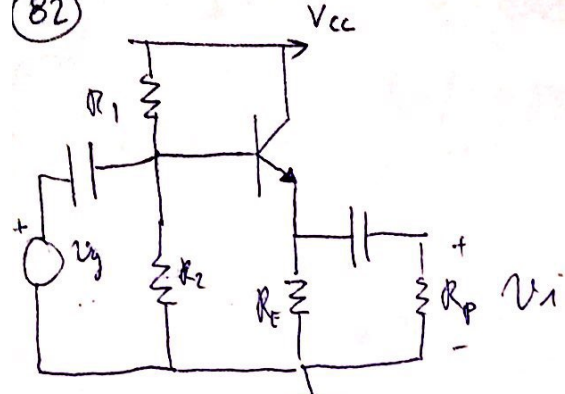

$$V_{TEV} = \frac{R_2}{R_1 + R_2} V_{CC} = 8V$$
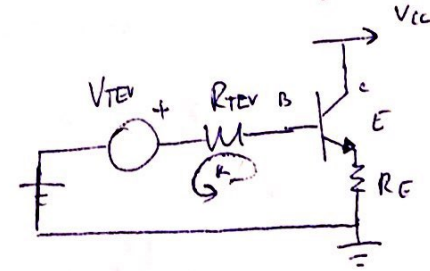
$$R_{TEV} = \frac{R_1 R_2}{R_1 + R_2} = 13k\Omega$$



$$(1 + \beta) i_B$$

$$i_E R_E + V_{BE} + i_B R_{TEV} = V_{TEV}$$

$$i_B = \frac{V_{TEV} - V_{BE}}{(1 + \beta) R_E + R_{TEV}} = 0,1 mA$$

$$I_C = \beta i_B = 10 mA$$

$$I_E = 10,1 mA$$


$$V_E = 6V$$

$$V_B = 6,7V \quad V_C = V_{CC} = 12V$$

$$g_m = \frac{I_C}{V_T} = 384,6 mS$$

$$r_{\pi} = \frac{\beta}{g_m} = 260 \Omega$$

$g_m V_{BE}$

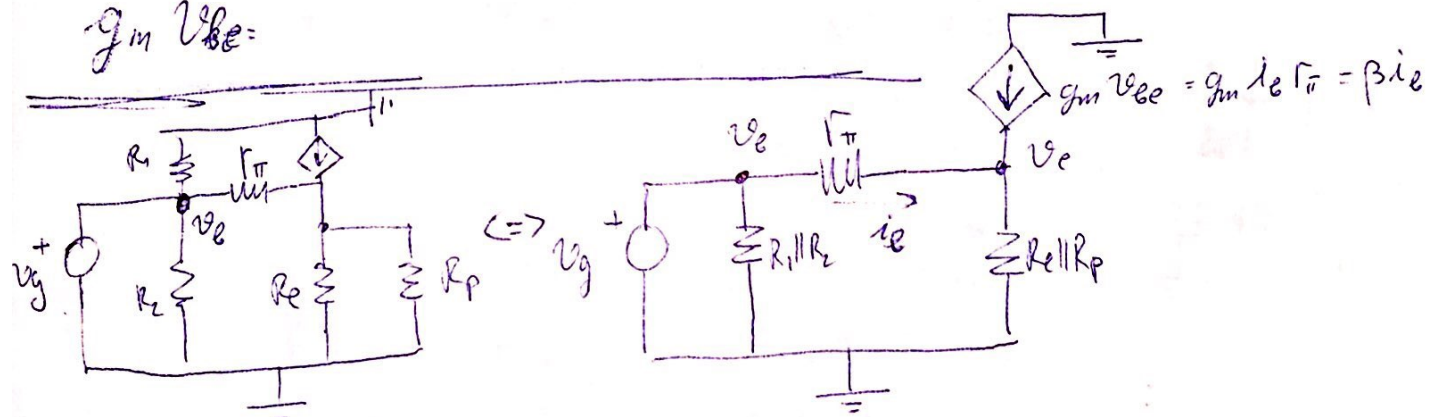

$$\beta i_B + \beta i_E = \frac{v_i}{R_E \parallel R_P}$$

$$i_E = \frac{v_g - v_i}{r_{\pi}}$$

$$i_E = \frac{v_i}{(1 + \beta) R_E \parallel R_P}$$

$$\frac{v_g - v_i}{r_{\pi}} = \frac{v_i}{(1 + \beta) R_E \parallel R_P}$$


$$v_i \left(\frac{1}{(1 + \beta) R_E \parallel R_P} - \frac{v_g}{r_{\pi}} \right) = 0$$

$$v_i = \frac{(1 + \beta) R_E \parallel R_P}{r_{\pi}} (v_g - v_i)$$

$$v_i \left(1 + \frac{(1 + \beta) R_E \parallel R_P}{r_{\pi}} \right) = v_g \cdot \frac{(1 + \beta) R_E \parallel R_P}{r_{\pi}}$$

$$v_i = v_g \cdot \frac{(1 + \beta) R_E \parallel R_P}{r_{\pi} + (1 + \beta) R_E \parallel R_P}$$
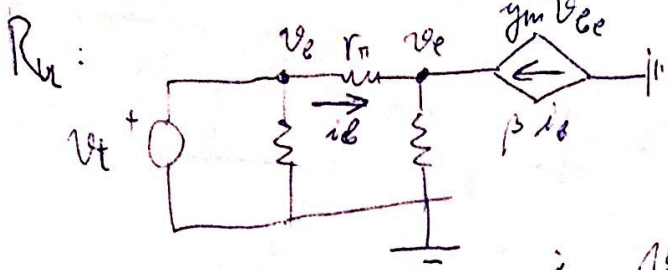
$$a = \frac{v_i}{v_g} = \frac{(1 + \beta) R_E \parallel R_P}{r_{\pi} + (1 + \beta) R_E \parallel R_P} \approx 0,993$$



$$i_t = \frac{v_t}{R_1 || R_2} + i_e$$

$$i_b = \frac{v_t - v_e}{r_{\pi}}$$

$$v_e = \frac{(1+\beta)i_b R_E || R_P}{R_E || R_P}$$

$$i_e = \frac{v_e}{(1+\beta)R_E || R_P}$$

$$\frac{v_e}{(1+\beta)R_E || R_P} = \frac{v_t - v_e}{r_{\pi}} \quad \therefore v_e = \frac{r_{\pi}}{(1+\beta)R_E || R_P + r_{\pi}} v_t$$

$$\frac{r_{\pi}}{(1+\beta)R_E || R_P} = \frac{v_t}{v_e} - 1 \quad v_e = v_t \left(\frac{(1+\beta)R_E || R_P}{r_{\pi} + (1+\beta)R_E || R_P} \right)$$

$$\frac{v_t}{v_e} = \frac{r_{\pi} + (1+\beta)R_E || R_P}{(1+\beta)R_E || R_P}$$

$$v_e = v_t \left(\frac{(1+\beta)R_E || R_P}{r_{\pi} + (1+\beta)R_E || R_P} \right)$$

$$(1+\beta)i_b + i_t = \frac{v_t}{R_E}$$

$$i_t = \frac{v_t}{R_E} - (1+\beta)i_b$$



$$i_b = -\frac{v_t}{r_{\pi}}$$

$$i_t = v_t \left(\frac{1}{R_E} + \frac{1+\beta}{r_{\pi}} \right)$$

$$R_{in} = \left(\frac{1}{R_E} + \frac{1+\beta}{r_{\pi}} \right)^{-1}$$

$$i_t = \frac{v_t}{R_1 || R_2} + v_t \left(1 - \frac{(1+\beta)R_E || R_P}{r_{\pi} + (1+\beta)R_E || R_P} \right)$$

$$R_{in} = \frac{v_t}{i_t} = \left(\frac{1}{R_1 || R_2} + \frac{1}{r_{\pi} + (1+\beta)R_E || R_P} \right)^{-1}$$

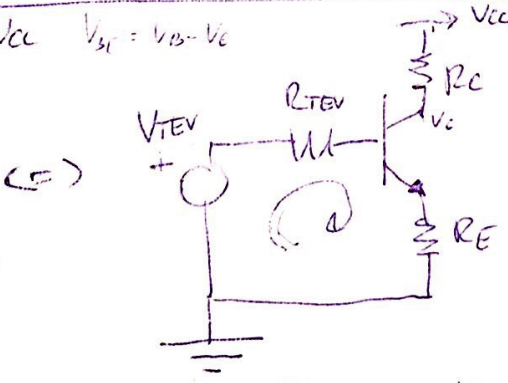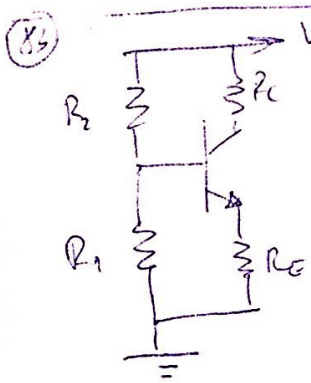

$$V_{TEV} = \frac{R_1}{R_1 + R_2} V_{CC}$$

$$R_{TEV} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{TEV} - V_{BE} = I_B (R_{TEV} + (1+\beta)R_E)$$

$$I_B = \frac{V_{TEV} - V_{BE}}{R_{TEV} + (1+\beta)R_E} = 16.57 \mu A$$

$$V_{TEV} - I_B \cdot R_{TEV} - V_{BE} - I_E \cdot R_E = 0 \quad I_C = 1.1657 \text{ mA} \quad I_E = 1.1674 \text{ mA}$$



$$I_E = I_B + I_C$$

$$I_C = \beta I_B$$

$$V_E = I_E R_E$$

$$V_B = V_{BE} + V_E$$



$$V_C = V_{CC} - R_C I_C$$

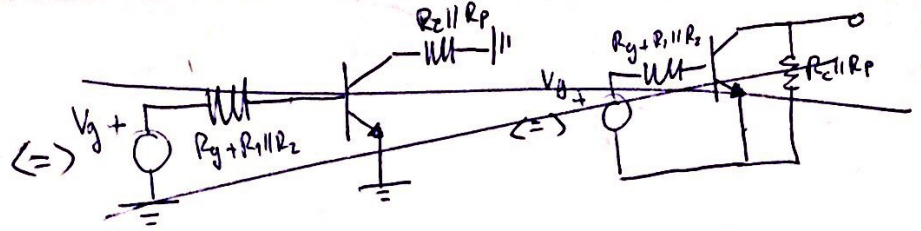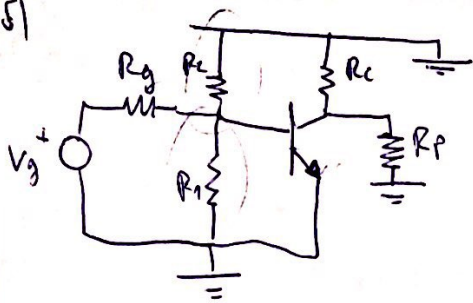

~~Handwritten scribble~~

$$V_{TEV} = \frac{R_1 || R_2}{R_g + R_1 || R_2} V_g$$

$$R_{TEV} = R_g || R_2 || R_3$$

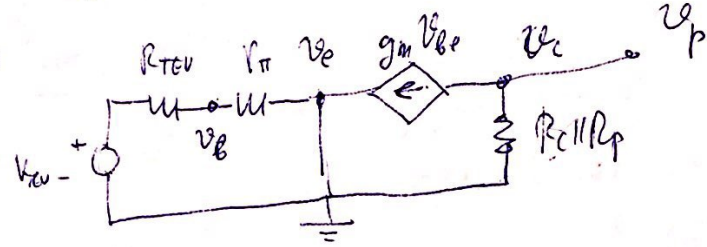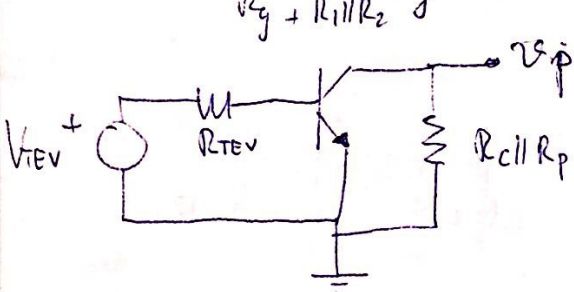

$$V_p = -g_m V_{ce} \cdot R_c || R_p$$

$$V_{ce} = \frac{r_{\pi}}{R_{TEV} + r_{\pi}} \cdot V_{TEV}$$

$$V_p = -\frac{I_c}{V_E} \cdot \frac{r_{\pi}}{R_{TEV} + r_{\pi}} \cdot R_c || R_p \cdot \frac{R_1 || R_2}{R_g + R_1 || R_2} \cdot V_g$$

$$A_v = -\frac{I_c}{V_E} \cdot \frac{r_{\pi}}{R_{TEV} + r_{\pi}} \cdot R_c || R_p \cdot \frac{R_1 || R_2}{R_g + R_1 || R_2}$$

$$R_{in} = R_g + R_1 || R_2 || r_{\pi}$$


$$R_{out} = R_c$$

$$V_{be} = 0$$

$$g_m V_{be} = 0$$



84) $\beta = 50$

DC:

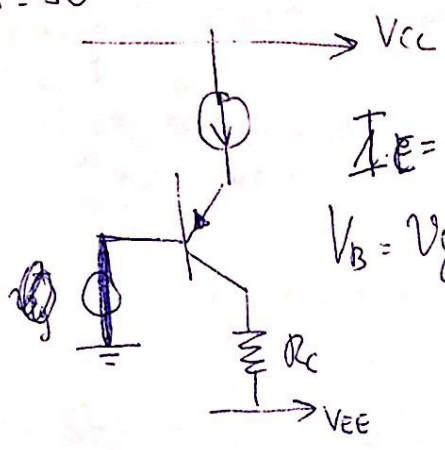

$I_E = I_R$
 $V_B = V_g$
 $I_B = \frac{I_E}{1 + \beta}$
 $I_C = \frac{\beta}{1 + \beta} I_E$
 $V_C = I_C R_C + V_{EE}$
 $V_{EB} = V_E - V_B$
 $V_E = V_{EB}$

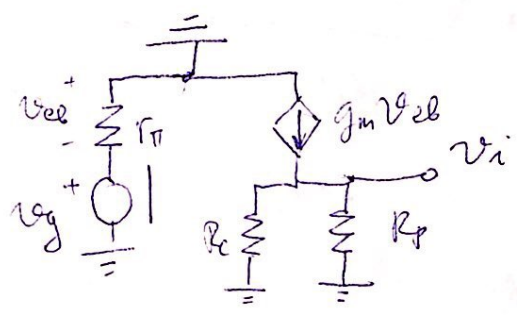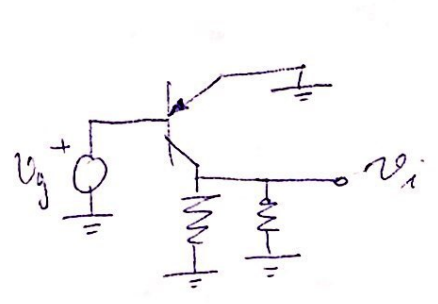$g_m = \frac{I_C}{V_T}$ $r_{\pi} = \frac{\beta}{g_m}$




$V_i = g_m V_{eb} \cdot R_c \parallel R_p$ $V_{eb} = -V_g$

$V_i = -g_m V_g \cdot R_c \parallel R_p$ $a = -g_m R_c \parallel R_p$

$R_{in} = r_{\pi}$

$R_{out} = R_c$

85

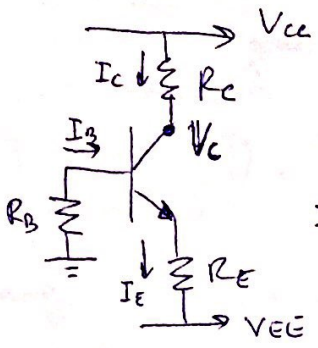

$$V_{EE} + I_E R_E + V_{BE} + I_B R_B = 0 \quad I_B = - \frac{V_{EE} + V_{BE}}{(1+\beta)R_E + R_B}$$

$$0 = I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0$$

$$I_B = \frac{V_{EE} - V_{BE}}{(1+\beta)R_E + R_B}$$

$$I_E = (1+\beta)I_B$$

$$I_B((1+\beta)R_E + R_B) = V_{EE} - V_{BE}$$

$$V_{EE} + (1+\beta)I_B R_E + V_{BE} + I_B R_B = 0$$

$$g_m = \frac{I_C}{V_T} = 33,72 \text{ mS}$$

$$I_B = - \frac{V_{EE} + V_{BE}}{(1+\beta)R_E + R_B} = 8,43 \mu\text{A}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

$$I_C = 843 \mu\text{A} \quad I_E = 851,4 \mu\text{A}$$

$$V_E = I_E R_E + V_{EE} = -0,996 \text{ V}$$



$$V_{BE} = V_B - V_E$$

$$V_B = V_{BE} + V_E = -0,396 \text{ V}$$

$$\frac{V_{CC} - V_C}{R_C} = I_C$$

$$V_C = V_{CC} - R_C I_C = 1,038 \text{ V}$$

Vce =

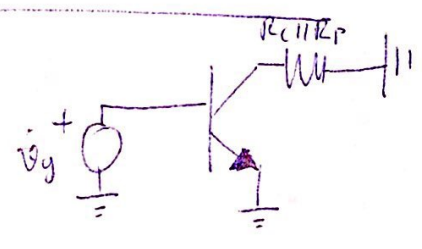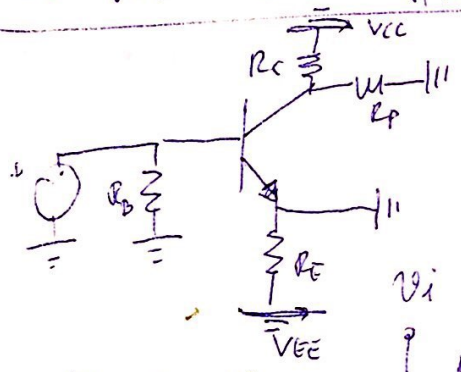

$$R_C || R_P = \frac{R_C R_P}{R_C + R_P} \approx 1,2 \text{ k}\Omega$$


$$\frac{0 - v_i}{R_C || R_P} = g_m v_{be}$$


$$v_i = -g_m v_{be} R_C || R_P$$

$$-a = -g_m R_C || R_P \approx -108$$

$$R_{in} = R_B || r_{\pi}$$

$$R_{out} = R_C$$

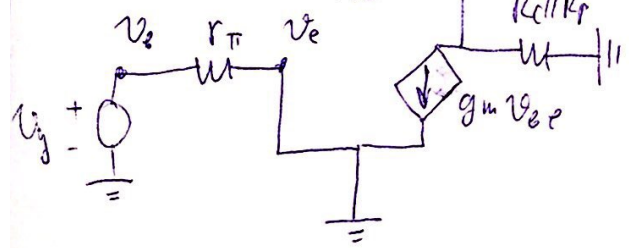

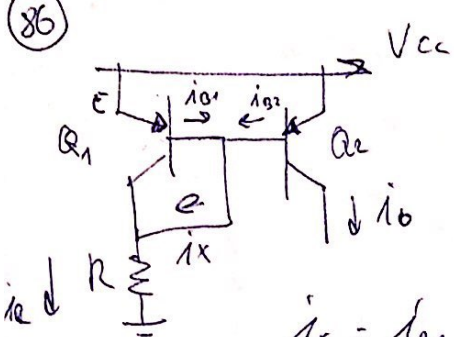

$$i_{C1} = i_{C2} = i_O$$

$$\Downarrow$$


$$i_{B1} = i_{B2}$$

$$i_X = i_{B1} + i_{B2} = 2i_B$$

$$i_R = i_{C1} + 2i_B = i_O(2 + \beta)$$

$$i_B = \frac{i_R}{2 + \beta} \quad i_O = \frac{\beta i_R}{2 + \beta} = \frac{\beta}{2 + \beta} \cdot \frac{V_{CC} - V_{BE}}{R}$$

87

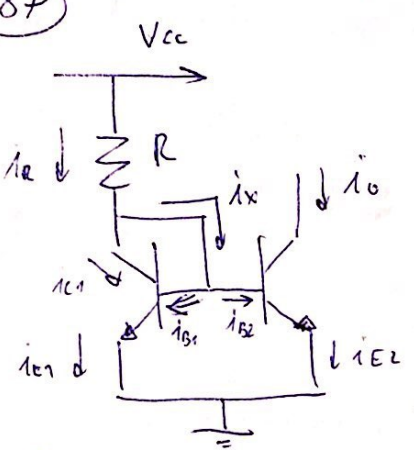

$$i_{C1} = i_{C2} = i_O$$

$$i_X = i_{B1} + i_{B2} = 2i_B$$


$$i_R = i_{C1} + 2i_B$$

$$i_O = i_R - 2i_B$$

$$i_R = i_B(\beta + 2)$$

$$i_C = \frac{\beta}{\beta + 2} i_R = \frac{\beta}{2 + \beta} \cdot \frac{V_{CC} - V_{BE}}{R}$$

88

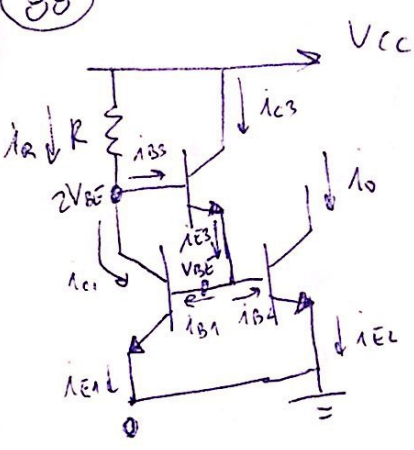

$$i_{C1} = i_{C2} = i_O$$

$$i_{C3} = 2i_B$$

$$(1 + \beta) i_{B3} = 2i_B$$

$$i_R = i_{B3} + i_{C1}$$

$$i_R = \frac{V_{CC} - 2V_{BE}}{R}$$

$$i_{B3} = \frac{2}{1 + \beta} i_B$$

$$i_B = \frac{(1 + \beta) i_{B3}}{2} \quad i_{C1} = \beta i_B = \frac{\beta(1 + \beta) i_{B3}}{2}$$

$$i_R = i_{B3} + \frac{\beta(1 + \beta) i_{B3}}{2} = i_{B3} \left(1 + \frac{\beta(1 + \beta)}{2} \right)$$

$$i_R = \frac{2}{1 + \beta} i_B + \beta i_B \Rightarrow i_B = \frac{i_R}{\left(\frac{2}{1 + \beta} + \beta \right)}$$

$$i_C = \beta i_B = \frac{V_{CC} - 2V_{BE}}{R \left(1 + \frac{2}{\beta(1 + \beta)} \right)}$$