

B
1

$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2} = 3k\Omega$$

$$R_{12} = 3k\Omega$$

$$R_{23} = 3k\Omega$$


$$I_1 = -\frac{1.5V}{3k\Omega} = -\frac{1}{2}mA = -0.5mA$$

$$I_3 = -\frac{1.8V}{3k\Omega} = -0.6mA$$

$$I_2 = \frac{1.8V - 1.5V}{3k\Omega} = 0.1mA$$

① a) $I = +1A$ d) $V = 2V$ $I = +2A$ b) $V = 1V$ $I = -1A$ ② a) \rightarrow d) \leftarrow b) \rightarrow
 $V = 10V$

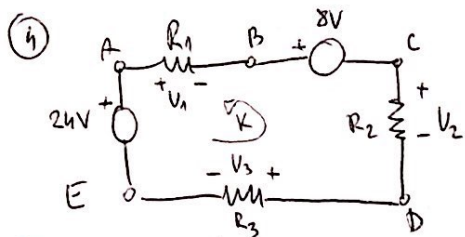③ a) $P_A = 6W$ $P_B = -6W$ d) $P_C = -30W$ $P_D = 30W$



$$V_1 = 9V$$

$$V_2 = 5V$$

$$V_3, U_{BE}, U_{DB}$$

$$U_{BE} = 15V$$


$$U_{DB} = -13V$$

$$V_3 + V_2 + 8V + U_1 - 24V = 0$$

$$V_3 = 16V - V_1 - V_2 = 16V - 9V - 5V = 2V$$

$$V_3 = 2V$$
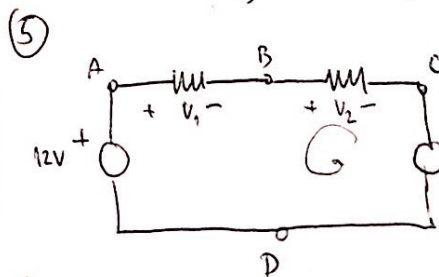
$$\begin{array}{r} 1 \\ 27 \\ \hline 36 \\ 63 \\ \hline 12 \\ 9 \end{array}$$



$$U_2, U_{BD} = ?$$


$$V_1 = 4V$$

$$U_2 + U_1 - 12V - 6V = 0$$

$$U_2 = 14V$$

$$6V$$

$$U_{BD} = 8V$$

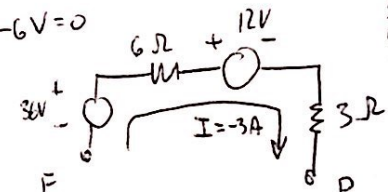

$$-3V + 12V - 18V - 36V = 9V$$

⑥ $V_1 = 1V$ $V_2 = 4V$ $V_3 = 2V$ $U_A, U_B = ?$ $U_A = 12V + V_1 = 13V$

$$U_B = V_3 - 24V = -22V$$

$$U_4 + 24V - V_3 - V_2 - U_1 - 12V = 0$$

$$U_4 = V_1 + V_2 + V_3 - 12V = 7 - 12 = -5V$$

⑦ a) $36V - I \cdot 6\Omega - 12V - I \cdot 3\Omega - I \cdot 2\Omega - I \cdot 1\Omega = 0$

$$I(6 + 3 + 2 + 1) = 24V \quad \boxed{I = 2A} \quad \frac{36}{22}$$

$$U_{BE} = -2V + 36V - 12V = 22V$$

$$U_{FD} = 2 \cdot 3V + 12V + 2 \cdot 6V - 36V = -6V$$

$$U_{FD} = -3I = 9V$$

$$P_{36V} = 72W$$

$$P_{3\Omega} = 12W$$

b) $36 - I(6 + 3 + 2 + 1) - 72 = 0$ $P_{3\Omega} = 27W$

$$I = -\frac{36}{12} = -3A$$

$$18 + 36 + 3$$

$$U_{FD} = 3I + 12V + 6V - 36V$$

$$P_{36V} = -108W$$

$$U_{BE} = -I \cdot 1\Omega + 36V - I \cdot 6\Omega = 57V$$


$$U_{FD} = 36V + 6 \cdot (-3A) + 12V + 3 \cdot (-3A) = -24V + 27V = 3V$$

8) $-I(1\Omega + 2\Omega + 3\Omega) - 30V + 18V = 0 \quad V_{out} = -4V$
 $6I = -12A \quad I = -2A \quad P_{30V} = 60W$

9) $I, V_{AC}, V_{BC}, P_{6\Omega}, P_{30V} \quad V_{AC} = 72V - 6V = 66V$

8) $-I(4 + 6 + 2) + 36V = 0 \quad V_{BC} = -36V - 18V = -54V$
 $I = 3A \quad P_{6\Omega} = 54W \quad P_{30V} = -108W$

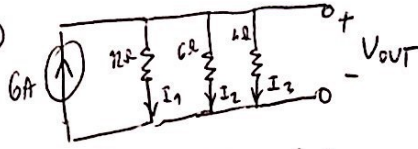10) $V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$



$V_{out} + 2V_{out} + 3V_{out} = 72V$

5) $-12A \uparrow$

$6V_{out} = -144V$

$V_{out} = -24V$

$I_1 = -2A \quad I_2 = -4A \quad I_3 = -6A$

$P_{20A} = 480W \quad P_{6\Omega} = 144W$

$I_1 + I_2 + I_3 = 6A$

$\frac{V_{out}}{12} + \frac{V_{out}}{6} + \frac{V_{out}}{4} = 6 \quad | \cdot 12$

$P_{20A} = -24W$
 $P_{6\Omega} = 36W$

$6V_{out} = 72V$


$V_{out} = 12V$

$I_1 = 1A$

$I_2 = 2A$

$I_3 = 3A$

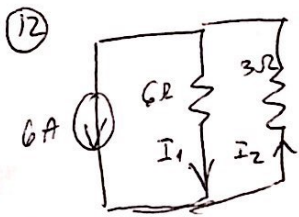13) $I_{out} = \frac{R_1}{R_1 + R_2} I_{in}$



$I_2 = \frac{2}{9} \cdot 6 = 4A$

$I_1 = -2A$

$V_{out} = -12V$

$P_{6\Omega} = 24W$

14) $6\Omega || 12\Omega = \frac{1}{\frac{2}{6} + \frac{1}{12}} = \frac{12}{3} = 4\Omega$

$R_e = 18\Omega$



$9\Omega || 18\Omega = \frac{1}{\frac{2}{18} + \frac{1}{18}} = 6\Omega$

$2\Omega || 2\Omega = 1\Omega$

$2\Omega || 2\Omega = 1\Omega$


$R_e = 7\Omega$

15) $6\Omega || 3\Omega = \frac{6 \cdot 3}{9} = 2\Omega$

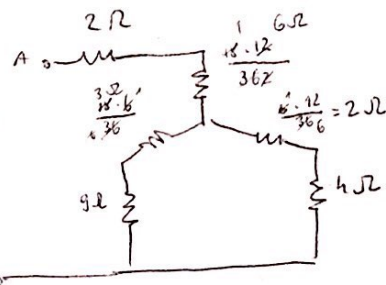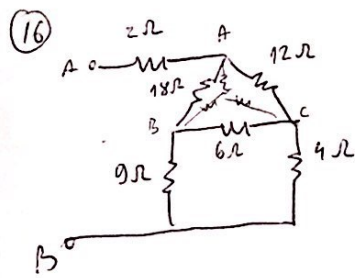


$12\Omega || 6\Omega = \frac{12 \cdot 6}{12 + 6} = \frac{12 \cdot 6}{18} = 4\Omega$

$R_e = 12\Omega$

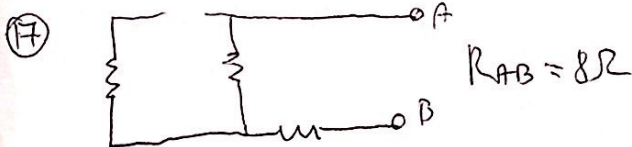

$R_{AB} = 8\Omega$

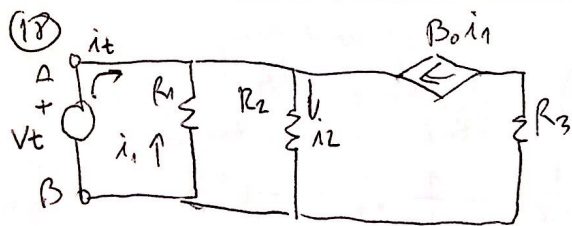

$$-i_1 R_1 = V_t$$

$$-i_1 = \frac{V_t}{R_1} \quad I = \frac{V}{R}$$

$$V_t = i_2 R_2$$

$$i_2 = \frac{V_t}{R_2}$$

$$i_t + i_1 + \beta_0 i_1 - i_2 = 0$$

$$i_1(1 + \beta_0) - i_2 + i_t = 0$$

$$i_t = i_2 - i_1(1 + \beta_0)$$

$$i_t = \frac{V_t}{R_2} + \frac{V_t(1 + \beta_0)}{R_1}$$

$$R_e = \frac{V_t}{i_t} = \frac{1}{\frac{1}{R_2} + \frac{1 + \beta_0}{R_1}} = \frac{R_1 R_2}{R_1 + R_2(1 + \beta_0)}$$

B 1

