


3. U kolu sa slike, na kružnoj učestanosti $\omega=10$ krad/s, uspostavljen je prostoperiodični režim i poznato je $u_G(t) = 4V \cos(\omega t + 45^\circ)$ i $i_G(t) = 1A \sin(\omega t)$. Potrebno je izračunati:

a) [4] impedansu Z_x ;

b) [18] struje $i_{L..5}$ u kompleksnom domenu za referentne smerove označene na slici;

c) [18] struje $i_{1..5}(t)$ u vremenskom domenu za referentne smerove označene na slici

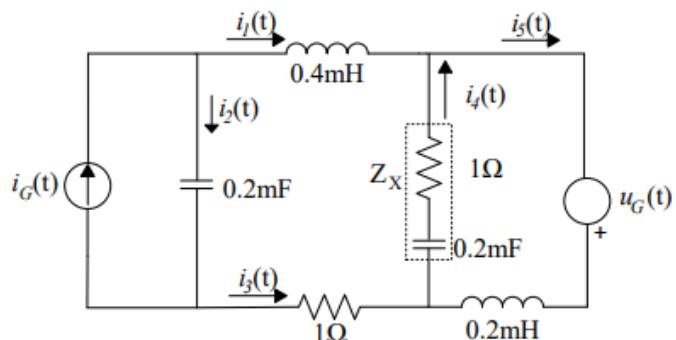d) [10] aktivnu, reaktivnu i kompleksnu snagu koja se razvija na impedansi Z_x .



$\text{U}_G(t) = 4V \cos(\omega t + 45^\circ)$ $\text{U}_G = 2\sqrt{2} \angle 45^\circ$
 $i_G(t) = 1A \sin(\omega t)$ $i_G = \frac{1}{\sqrt{2}} \angle -70^\circ$
 $\omega = 10 \text{ rad/s}$

a) $Z_x = 1\Omega - j \frac{1}{0.2\mu\text{F} \cdot 0.2\text{mH}} = 1\Omega - j \frac{1}{0.0002 \cdot 0.0002} = (1 - j \frac{1}{2}) \cdot 10^6$

b) $\text{U}_G = 2\sqrt{2} \cdot \left(\frac{\sqrt{2}}{2} + j \frac{\sqrt{2}}{2} \right) = (2 + j2) \text{V}$, $\text{I}_G = \frac{\sqrt{2}}{2} \cdot -j = -j \frac{\sqrt{2}}{2}$, $\text{X}_{\text{cap}} = -j \frac{1}{2} \cdot 0$, $\text{X}_{\text{ind}} = j4\Omega$, $\text{Y}_{\text{load}} = j2\Omega$

$\text{U}_1 = \frac{1}{1+j0.5} \cdot \left(\frac{1}{1+j0.5} + \frac{1}{j2} \right) = \frac{-\sqrt{2}}{1+j0.5} - \frac{2+j2}{2j}$

$\text{U}_2 = \frac{1-j0.5}{1+j0.5} + \frac{1+j0.5}{1+j0.5} - \frac{j}{2} = \frac{-\sqrt{2}}{4+j4} + j(-1+j)$

$\text{U}_3 = \frac{1-j0.5}{1+j0.5} + \frac{1+j0.5}{1+j0.5} - \frac{j}{2} = \frac{-\sqrt{2} \cdot (4-j4)}{16+16} + j(4+j0)$

$\text{U}_4 = \frac{4-j4}{5j} + \frac{4+j2}{5} - \text{a}_1 \text{I}_2 = \frac{-\sqrt{2} \cdot 4 + j4\sqrt{2}}{2 \cdot 12} + j(1+j)$

$\text{U}_5 = \frac{(16-j56) + j4(4+2j) - 10j}{5 \cdot 2 \cdot 12} = \frac{-10\sqrt{2} + j4\sqrt{2} - 24\Omega + 2j\Omega}{2 \cdot 12}$

$\text{U}_6 = (16-j56 + \frac{8(4+2j)}{5} - 10\Omega) = -4\sqrt{2} - 24\Omega + j24\Omega + j14\Omega$

$\text{U}_7 = (185.6 - 77j2j) = -217.66 + j231.8$

$\text{U}_8 = \frac{-217.66 + j231.8}{185.6 - 77j2j} = \frac{-217.66 + j231.8 \cdot (185.6 + 77j2j)}{40500 + 12} = -1.54 - j0.65$

$\text{I}_1 = \frac{\text{U}_6 - \text{U}_1}{1+j0.5} = \frac{-\sqrt{2} + 1.54 - j0.65}{1+j0.5} = \frac{(1.05 - j0.65)(1-j0.5)}{13/25} = -0.03 - j0.337$

$\text{I}_2 = -\text{I}_1 = 0.03 + j0.337$

$\text{I}_2 = \text{I}_9 - \text{I}_1 = -j \frac{\sqrt{2}}{2} + 0.03 + j0.337 = 0.03 - j0.337$

~~$\text{I}_3 = \frac{\text{U}_2 - \text{U}_1}{j2} = \frac{-1.44 - j0.65}{j2} = \frac{(-1.44 - j0.65)(1+j0.5)}{j2} = 1.492 + j0.056$~~

$\text{I}_3 = \frac{-\text{U}_1}{j2} = -1.44 - j0.65 = \frac{(-1.44 - j0.65)(1+j0.5)}{j2} = 1.492 + j0.056$

$\text{I}_4 = \frac{\text{U}_5 + \text{U}_6}{2j} = \frac{-1.44 + j4.65 + 2+j2}{2j} = \frac{0.56 + j2.65}{2j} = 1.325 - j0.026$

$\text{I}_5 = 0.35\sqrt{2} \cdot \cos(\omega t - 10^\circ)$ $S = \frac{1}{2} \cdot \text{I}_5^2 = ((1.42 + j0.056)^2 \cdot (1-j0.5)) = (2 + 0.16j)(1-j0.5)$

$\text{I}_6 = 0.38\sqrt{2} \cdot \cos(\omega t - 26.35^\circ)$ $P = 2.08 \text{ W}$

$\text{I}_7 = 0.35\sqrt{2} \cdot \cos(\omega t + 7.5^\circ)$ $Q = -0.84 \text{ VAr}$


$\text{I}_8 = 2.41\sqrt{2} \cdot \cos(\omega t + 22.2^\circ)$

$\text{I}_9 = 1.35\sqrt{2} \cdot \cos(\omega t - 17.9^\circ)$

Kolokvijum 2 2020

2. U kolu sa slike uspostavljen je prostoperiodični režim i poznato je $u_g(t) = 8\sqrt{2}\cos(\omega t + 45^\circ)$ i $i_g(t) = 8A\sin(\omega t)$ gde je $\omega = 10\text{krad/s}$. Potrebno je:

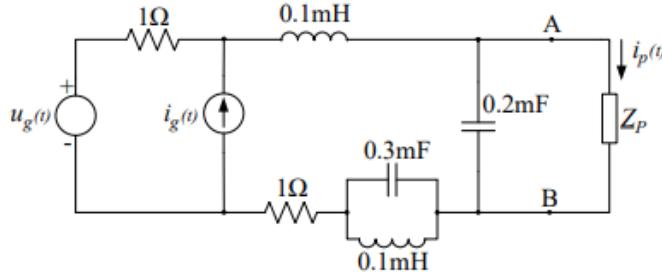- a) [11] za deo kola levo od tačaka A i B izračunati parametre Tevenenovog generatora u kompleksnom domenu;
- b) [4] za parametre izračunate pod tačkom a) izračunati ekvivalentni Tevenenov generator u vremenskom domenu;
- c) [2] odrediti impedansu Z_p tako da se na njoj razvija maksimalna aktivna snaga;
- d) [3] za impedansu izračunatu pod tačkom c) odrediti struju $i_p(t)$ u vremenskom domenu.



$$\begin{aligned}
 & u_g(t) = 8\sqrt{2} \cos(\omega t + 45^\circ) \\
 & i_g(t) = 8A \sin(\omega t) \\
 & \omega = 10 \cdot 10^3 \text{ rad/s} \\
 & U_g = 8 \angle 45^\circ \\
 & I_g = 8A \sin \omega t \\
 & U_g = 8 \cdot (\cos 45^\circ + j \sin 45^\circ) \\
 & U_g = 8 \cdot \frac{\sqrt{2}}{2} + j 4\sqrt{2} \\
 & U_g \approx 4\sqrt{2} + j 4\sqrt{2} \\
 & X_{L_{01}} = j \cdot \omega L = j \cdot 10 \cdot 10^3 \cdot 0.1 \cdot 10^{-3} \\
 & X_{L_{01}} = j \cdot 1000 \\
 & X_{C_{03}} = -j \cdot \frac{1}{\omega C} = -j \frac{1}{0.3 \cdot 10^{-3} \cdot 10 \cdot 10^3} = -j \frac{1}{3} \Omega \\
 & X_{C_{02}} = -j \frac{1}{\omega C} = -j \frac{1}{2} \Omega \\
 & X_{L_{02}} = j \cdot 1000 \\
 & X_{L_{02}} = \frac{-j \frac{1}{2} \Omega - j \frac{1}{3} \Omega}{j \frac{1}{2} \Omega} = -j \frac{1}{2} \Omega \\
 & V_{AB} = I_{AB} \cdot X_{C_{02}} = \frac{U_g}{1\Omega + j \frac{1}{2} \Omega - j \frac{1}{3} \Omega + j \frac{1}{2} \Omega} = (-j 0.5) = \frac{4\sqrt{2} + j 4\sqrt{2}}{2} = 2\sqrt{2} + j 2\sqrt{2} \\
 & V_{AB} = \frac{1}{2} \cdot j \frac{1}{2} \cdot (-j 0.5) = -j 2\sqrt{2} (-j 0.5) \\
 & V_{AB} = 2\sqrt{2} (-j 0.5) = -j \sqrt{2} \\
 & Z_{TEV} = \frac{(1\Omega + j \frac{1}{2} \Omega + j \frac{1}{3} \Omega - j \frac{1}{2} \Omega)(-j 0.5)}{2\sqrt{2}} = \frac{(2 + j 0.5\Omega)(-j 0.5\Omega)}{2\sqrt{2}} \\
 & Z_{TEV} = \frac{-j + 0.25}{2} = 0.125 - j 0.125 \quad | = \frac{1}{8} - j \frac{1}{20} \\
 & U_{AB} = V_2 \cdot (\cos(\omega t) + j \sin(\omega t)) \\
 & U_{AB} = 2 \cdot \cos(\omega t - 90^\circ) \\
 & U_{AB} = 2 \cdot \sin(\omega t) \\
 & R_{TEV} = \frac{1}{Z_{TEV}} = 0.2 \text{ mF} \\
 & Z_0 = Z_{TEV} = \frac{1}{8} + j \frac{1}{2} \Omega \\
 & I_p = \frac{U_{TEV}}{2 \cdot \frac{1}{8}} = j 4\sqrt{2} \\
 & I_p = 8A \sin \omega t
 \end{aligned}$$

Februar 2019


3. Kolo naizmenične struje sa slike radi u ustaljenom prostoperiodičnom režimu na frekvenciji $f = 50\text{kHz}$. Poznato je da je $u_{g1}(t) = 2\text{V} \cos(2\pi ft + 45^\circ)$, $u_{g2}(t) = -2\sqrt{2}\text{V} \sin(2\pi ft)$, $i_{g1}(t) = 2\text{A} \cos(2\pi ft - 45^\circ)$ i $i_{g2}(t) = -\sqrt{2}\text{A} \sin(2\pi ft)$.

a) [60] Odrediti parametre ekvivalentnog Nortonovog generatora u kompleksnom domenu za deo kola levo od tačaka A i B.

b) [10] Odrediti elemente (i vrednosti elemenata) koji treba da sačinjavaju potrošač Z_p , tako da se na njemu razvija maksimalna aktivna snaga.

c) [20] Pod uslovom iz tačke b) odrediti kompleksnu, aktivnu i reaktivnu snagu na potrošaču Z_p .

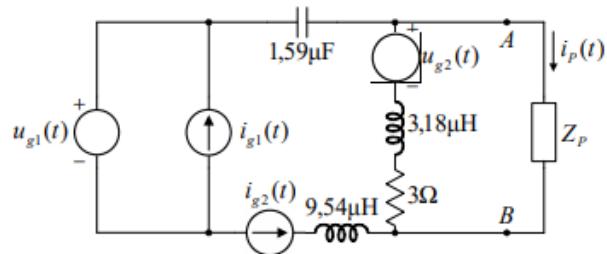d) [10] Pod uslovom iz tačke b) odrediti struju $i_p(t)$.



a)

$f = 50\text{kHz}$

$$U_{g1} = 2\text{V} \cos(2\pi ft + 45^\circ)$$

$$U_{g2} = -2\sqrt{2}\text{V} \sin(2\pi ft)$$

$$I_{g1} = 2\text{A} \cos(2\pi ft - 45^\circ)$$

$$I_{g2} = \sqrt{2}\text{A} \sin(2\pi ft)$$

$$X_C = \frac{-j}{100\pi f C} = -j2\Omega$$

$$X_L = j2\pi f L = j2\Omega$$

$$X_{L2} = j3\Omega$$

$$U_{AB} = U_{AB}^I + U_{AB}^{II} + U_{AB}^{III} + U_{AB}^{IV} = 0\text{V} + U_{g2} + 0\text{V} + (-I_{g2}(X_{L1} + R_1)) = 2j - j(3+j) = 1-j$$

$$Z_N = Z_{TEV} = R + X_{L1} = (3+j)\Omega$$

$$I_N = \frac{U_{AB}}{Z_{TEV}} = \frac{1-j}{3+j} \cdot \frac{3-j}{3-j} = \frac{3+1-3j-j}{10} = (0.12 - 0.14j) \text{A}$$

b)

$$Z_p = Z_N^* = 3-j$$

$$R_p = 3\Omega$$

$$C_p = 3.18\mu\text{F}$$

$$I_p = \frac{\sqrt{2}}{6} \left(\frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right)$$

$$I_{p(t)} = \sqrt{2} \cdot \frac{\sqrt{2}}{6} \cos(2\pi ft - 45^\circ)$$

$$I_{p(t)} = \frac{1}{3} \cos(100000\pi t - 45^\circ)$$

Resenja: Merisa Harcinovic