

① a)  $i_D = 200 \mu A$       $v_D = ?$


$$i_D = I_S \left( e^{\frac{v_D}{V_T}} - 1 \right)$$

$$e^{\frac{v_D}{V_T}} = \frac{i_D}{I_S} + 1 \quad / \ln$$

$$\frac{v_D}{V_T} = \ln \left( \frac{i_D}{I_S} + 1 \right) \quad v_D = V_T \ln \left( \frac{i_D}{I_S} + 1 \right)$$


$$v_D = 0.1823 \text{ V}$$
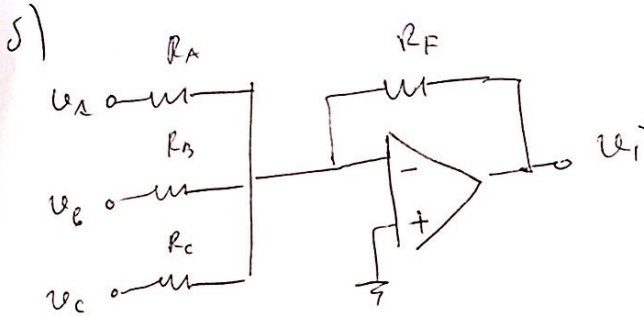
$$\frac{v_A}{R_A} + \frac{v_B}{R_B} + \frac{v_C}{R_C} = - \frac{v_i}{R_F}$$



$$v_i = - \left( \frac{R_F}{R_A} v_A + \frac{R_F}{R_B} v_B + \frac{R_F}{R_C} v_C \right)$$
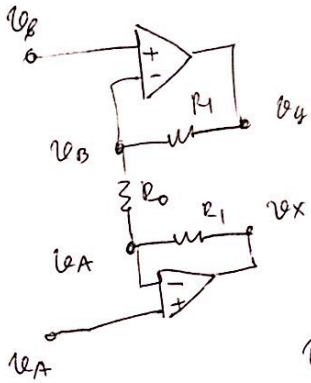
$$R_A = 15 \text{ k}\Omega \quad R_B = 5 \text{ k}\Omega \quad R_C = 3 \text{ k}\Omega$$



$$\frac{v_y - v_B}{R_1} = \frac{v_B - v_A}{R_0}$$

$$v_y - v_B = \frac{R_1}{R_0} v_B - \frac{R_1}{R_0} v_A$$

$$v_y = \left( \frac{R_1}{R_0} + 1 \right) v_B - \frac{R_1}{R_0} v_A$$

$$\left( \frac{2R}{R_0} + 1 \right) = 10$$

$$\frac{2R}{R_0} = 9$$

$$R_0 = \frac{2}{9} R$$

$$R_0 = 21.22 \text{ k}\Omega$$

$$\frac{v_B - v_A}{R_0} = \frac{v_A - v_x}{R_1}$$

$$\frac{v_x - v_A}{R_1} = \frac{v_A - v_B}{R_0} \quad v_x - v_A = \frac{R_1}{R_0} v_A - \frac{R_1}{R_0} v_B$$

$$v_x = \left( \frac{R_1}{R_0} + 1 \right) v_A - \frac{R_1}{R_0} v_B$$


$$v_i = \frac{R_3}{R_2} (v_x - v_y) = \frac{R_3}{R_2} \left( \left( \frac{R_1}{R_0} + 1 \right) v_A - \frac{R_1}{R_0} v_B - \left( \frac{R_1}{R_0} + 1 \right) v_B + \frac{R_1}{R_0} v_A \right)$$

$$= \frac{R_3}{R_2} \left( \left( \frac{2R_1}{R_0} + 1 \right) v_A - \left( \frac{2R_1}{R_0} + 1 \right) v_B \right) = \frac{R_3}{R_2} \left( \frac{2R_1}{R_0} + 1 \right) (v_A - v_B)$$

$$U_b = 8 \left( \frac{\sqrt{2}}{2} + \frac{\sqrt{2}}{2}j \right) = 4\sqrt{2}(1+j)$$

$$\frac{8}{\sqrt{2}} = \frac{8\sqrt{2}}{2} = 4\sqrt{2}$$

$$I_b = -4\sqrt{2}j$$

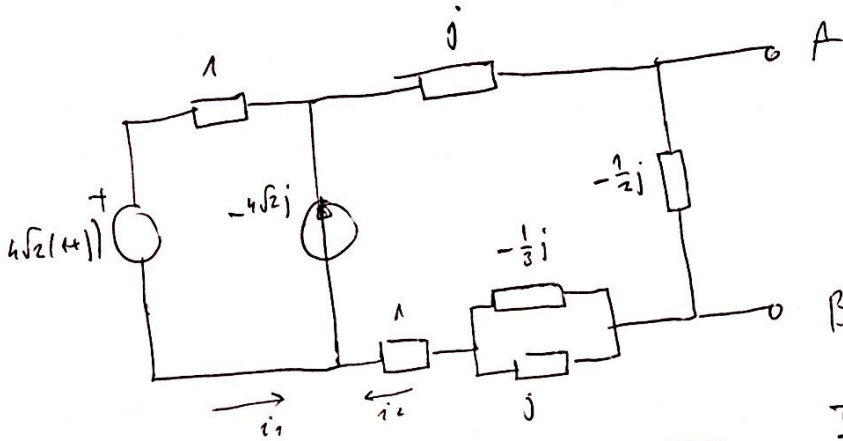

$$\Delta_{TEV} =$$

$$\frac{-\frac{1}{3}j - j}{\frac{2}{3}j} = \frac{\frac{1}{3}}{\frac{2}{3}} \cdot \frac{j}{j} = \boxed{-\frac{1}{2}j}$$

$$\left( 2 + \frac{j}{2} \right) \parallel \left( \frac{1}{2} + \frac{1}{2}j \right) =$$

$$\text{Ans } \boxed{i_1 + i_2 = -4\sqrt{2}j}$$

$$i_2 \left( 1 - \frac{1}{2}j - \frac{1}{2}j + j \right) - i_1 = 4\sqrt{2}(1+j)$$

$$i_2 - i_1 = 4\sqrt{2} + 4\sqrt{2}j$$

$$i_1 + i_2 = -4\sqrt{2}j$$

$$\boxed{U_T = -\frac{1}{2}j \cdot 2\sqrt{2} = -j\sqrt{2}}$$

$$2i_2 = 4\sqrt{2} \quad \boxed{i_2 = 2\sqrt{2}}$$

$$\frac{\left( 2 + \frac{j}{2} \right) \cdot \left( -\frac{1}{2}j \right)}{2 + \frac{j}{2} - \frac{1}{2}j} = \frac{-j + \frac{1}{4}}{2} = \underbrace{-\frac{1}{2}j + \frac{1}{8}}_{Z_t}$$

$$\left( 2 + \frac{j}{2} \right) \parallel \left( -\frac{j}{2} \right) = \frac{\left( 2 + \frac{j}{2} \right) \left( -\frac{j}{2} \right)}{2}$$

$$u_t(t) = 2 \sin(\omega t)$$

$$R_t = \frac{1}{8} \Omega \quad C_t = 0,2 \text{ mF}$$

$$\frac{-j\sqrt{2}}{\frac{1}{4}} = -4\sqrt{2}j = i_t$$



$$\boxed{32}$$

$$\boxed{i_t(t) = 8 \sin \omega t}$$

$$\boxed{Z_p = \frac{1}{8} + \frac{1}{2}j}$$

$$\frac{32}{8} + 16j$$

3

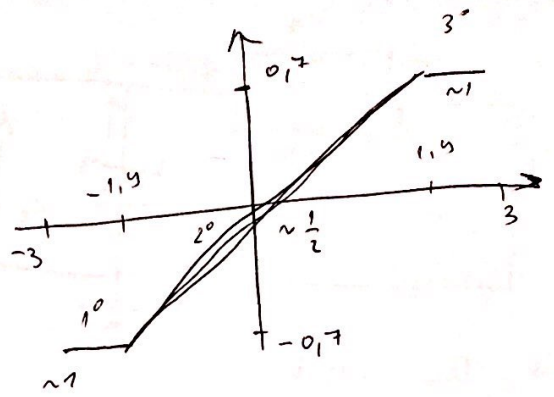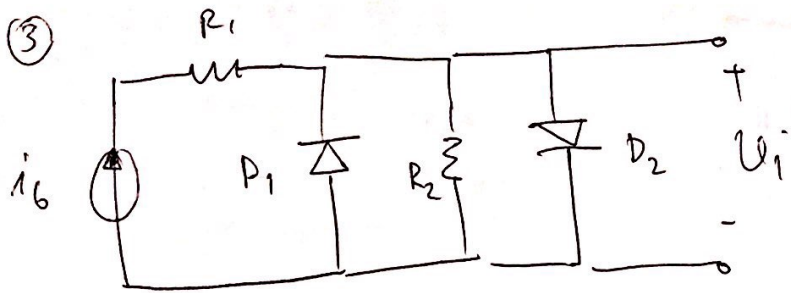

3a  $i_g = -3 \text{ mA}$

$D_1: \text{ON}, D_2: \text{OFF}$

$V_i = -V_D = -0.7 \text{ V}$  1°


$V_{D2} = -0.7 \text{ V}$  OFF je

$i_g \in (-3, -1.4)$

$i_{R2} = -1.4 \text{ mA}$

$i_{D1} = -i_g + i_{R2} = -i_g + 1.4 \text{ mA} > 0$

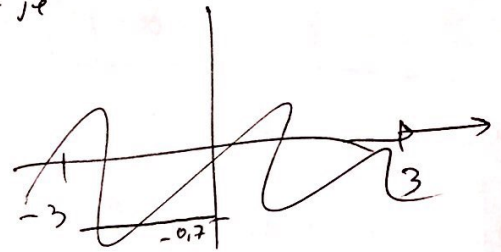3a  $i_g = -1.4 \text{ mA}$   $D_1 \rightarrow \text{OFF}$



$V_i = i_g R_2$  2°

$i_g \in (-1.4, 1.4)$

3a  $i_g R_2 = V_D$

3a  $i_g = 1.4 \text{ mA}$


$D_2 \rightarrow \text{ON}$

$V_i = V_D = 0.7 \text{ V}$  3°

$i_g \in (1.4, 3)$

$i_{R2} = 1.4 \text{ mA}$   $i_{D2} = i_g - 1.4 \text{ mA} \rightarrow$

$V_{D1} = -0.7 \text{ V}$

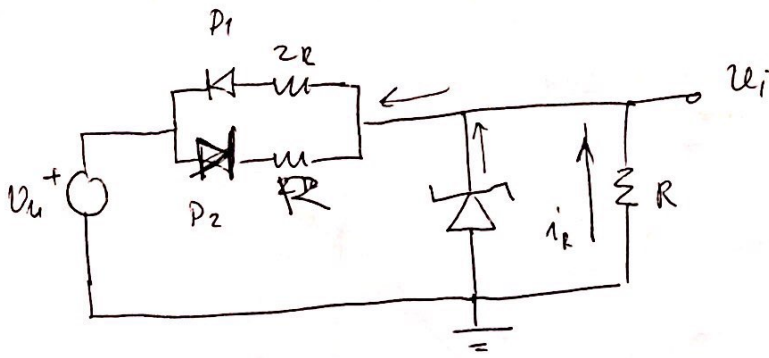

$$i_R + i_Z = i_{D1}$$

$$i_Z = i_{D1} - i_R$$

34  $U_u = -10V$   
 $D_2: ON, D_1: ON$

$$i_R = 0,6mA$$

$$V_i = -V_D = -0,6V \quad 1^{\circ} \quad U_{g \in (-10, -2,4)}$$

$$U_{D2} = U_u + 0,6V < 0$$

$$U_u + V_D + i_{D1} \cdot 3R = 0$$

$$i_{D1} = -\frac{U_u + V_D}{3R}$$

$$U_u + 0,6 + i_{D1} \cdot 2R + 0,6 = 0$$

$$V_i = +\frac{1}{3}U_u + 0,2 \quad 2^{\circ} \quad U_{g \in (-2,4, -0,6)}$$

$$i_{D1} = -\frac{U_u + 1,2V}{2R}$$


$$U_{D2} = U_u - V_i = U_u - \frac{1}{3}U_u - 0,2$$

$$i_Z = -\frac{U_u}{2} - 1,2mA$$

$$U_{D2} = \frac{2}{3}U_u - 0,2$$

39  $U_u = -2,4V$   $D_2: OFF$
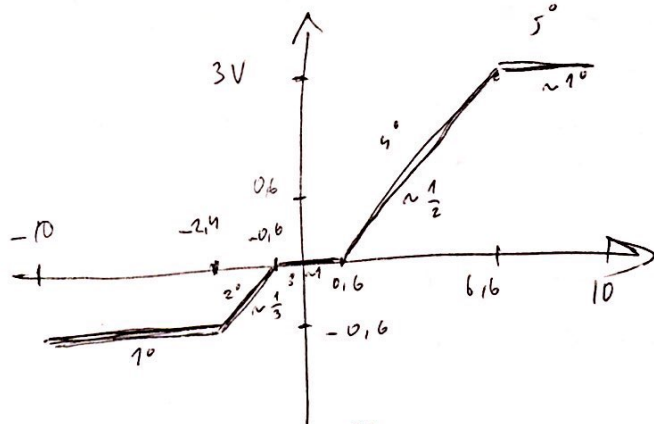
$$V_i = 0 \quad 3^{\circ} \quad U_{g \in (-0,6, 0,6)}$$




34  $U_{g} = 0,6V$   $D_2 \rightarrow ON$

$$V_2 + V_D + i_{D2}R = U_g$$

$$U_u + V_D - i_{D2} \cdot 2R = 0$$

$$i_{D2} = \frac{U_g - 3,6V}{R}$$

$$i_{D2} = \frac{U_u - V_D}{2R}$$

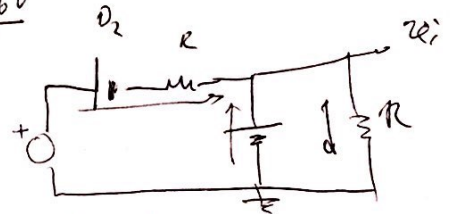


$$i_Z + i_D = i_R$$

$$V_i = \frac{U_u}{2} - 0,3 \quad 4^{\circ}$$

39  $U_i = 3V$   $U_u = 6,6V$   $D_2 \rightarrow \text{through}$

$$V_i = 3V \quad 5^{\circ}$$
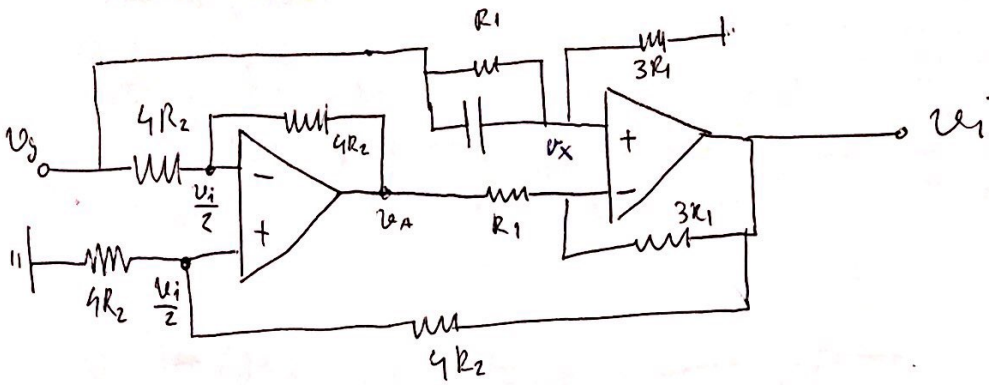
$$i_R = 3mA \quad i_Z = 3mA = \frac{U_g}{R} + 3,6mA = 6,6mA - \frac{U_g}{R}$$



AC:  $\frac{v_g - \frac{v_i}{2}}{4R_2} = \frac{v_i - v_A}{4R_2}$       $v_A = v_i - v_g$

$\frac{v_A - v_g}{R_1} = \frac{v_g - v_i}{3R_1}$

$3v_A - 3v_g - 3v_g = v_g - v_i$   
 $4v_i = 5v_g$   
 $v_i = \frac{5}{4}v_g$

$3v_A - 3v_g = v_g - v_i$

$v_i = 4v_g - 3v_A = 4v_g - 3v_i + 3v_g$

$4v_i = 7v_g$

$v_i = \frac{7}{4}v_g$

DC:

$v_A = v_i - v_g$

$\frac{v_g - v_x}{R_1} = \frac{v_x}{3R_1}$

$\frac{v_A - v_x}{R_1} = \frac{v_x - v_i}{3R_1}$

$v_g = \frac{4}{3}v_x$

$v_x = \frac{3}{4}v_g$

$3v_A - 3v_x = v_x - v_i$

$v_i = 4v_x - 3v_A = 3v_g - 3v_i + 3v_g$

$4v_i = 6v_g$   
 $v_i = \frac{3}{2}v_g$

$v_i = 6mV - 14mV \cos(\omega t)$

$v_A = v_i - v_g$

$3v_g - 3v_g = v_g - v_A$

$3v_g = 4v_g - v_A$

$3v_i - 3v_g = 4v_g - v_i$

$v_i = \frac{7}{4}v_g$